
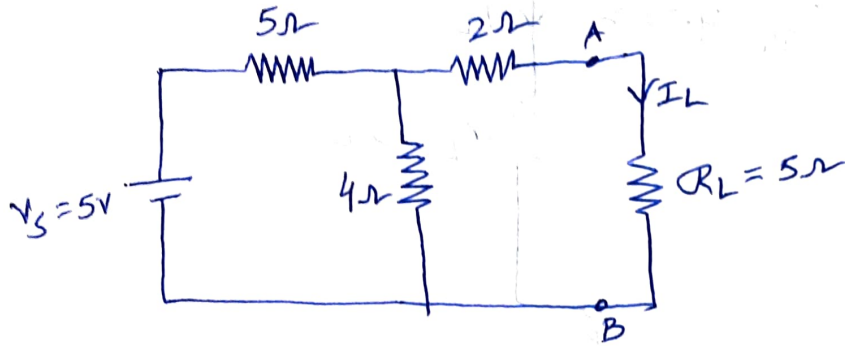


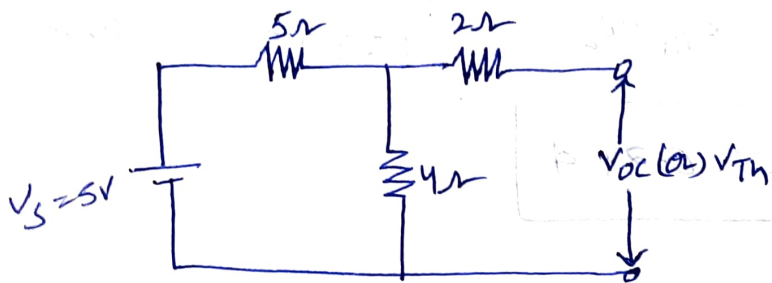① Find The current through ' $R_L$ ' by using Thevenin's Theorem.




$$I_L = ?$$

Step: 1: To find Thevenin's voltage ( $V_{Th}$  or  $V_{OC}$ )



$$\therefore V_{OC} \text{ (or) } V_{Th} = 5 \times \frac{4}{5+4} \Rightarrow \frac{20}{9} \text{ V} \Rightarrow 2.22 \text{ V}$$

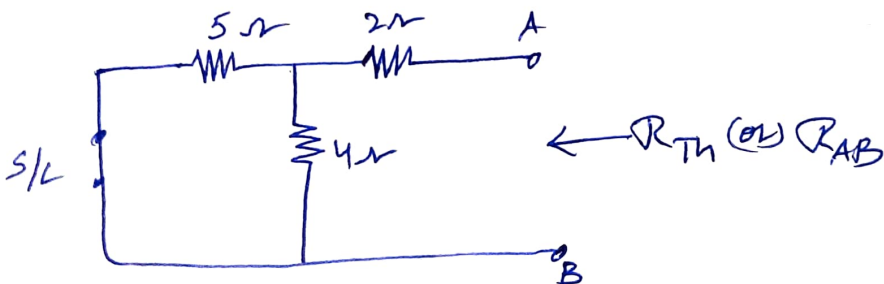
Step: 2 TO find Thevenin Resistance ( $R_{Th}$ ) :-



$$\therefore R_{Th} \text{ (or) } R_{AB} = (5 // 4) + 2$$

$$R_{Th} = \frac{20}{9} + 2 \Rightarrow \frac{38}{9} \Omega \Rightarrow 4.22 \Omega$$

Step 3: Thevenin's eq. CKT:-

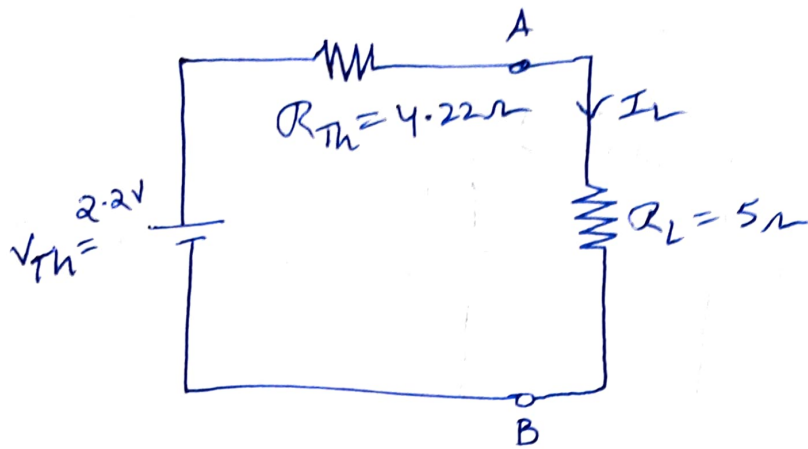

$$\therefore I_L = \frac{V_{TH}}{R_{TH} + R_L} = \frac{2.22}{4.22 + 5} \Rightarrow \frac{2.22}{9.22}$$

$$\Rightarrow \boxed{I_L = 0.24 A}$$