

27/7/22

### Unit - 3:


#### Rectifiers - And Filters:

For the operation of most of the electronic devices and circuit a DC source is required so it is advantageous to convert AC supply into DC Voltage.

The process of converting AC voltage into DC voltage is called as rectification.

This is achieved with the

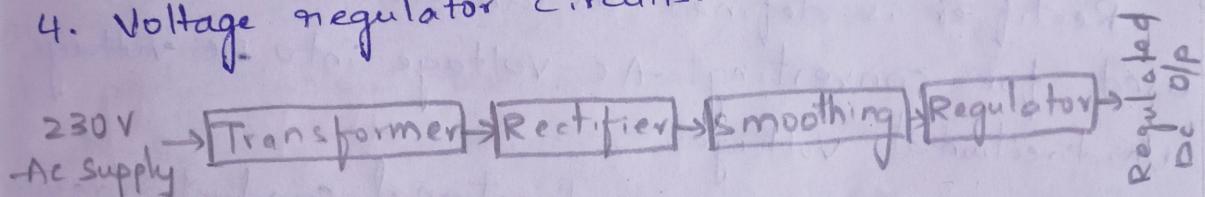1. Stepdown transformer
2. Rectifier
3. Filter / smoothing
4. Voltage regulator circuits.



→ Transformer:

Stepdown 230V Ac Supply to low Voltage

AC ~~rectifier~~

→ Rectifier:

Converts AC Voltage to DC Voltage but the Output is Varying

→ Filter.

Smooth the DC from varying greatly to small ripple. Regulator eliminates ripple by setting up DC output to a fixed value

→ P-N junction diode as a rectifier

A P-N junction diode is a two terminal device and it is polarity sensitive

When the diode is in forward bias then it conducts and allows current to flow through it with-out any resistance, then the diode is in on state.

When the diode is in reverse bias then it does not conduct and no current flows through it then the diode is in off state

Thus, an ideal diode acts as a switch either open or close depending upon the polarity of voltage placed across it

Ideal diode has zero resistance under forward bias and infinite resistance under reverse bias

Rectifier is defined as an electronic device used for converting AC voltage into DC voltage


Unidirectional Voltage

A rectifier utilizes unidirectional conduction devices like a P-N diode


→ Half wave rectifier

A half-wave rectifier is one which converts AC voltage in a pulsating voltage using only half cycle of the applied AC voltage

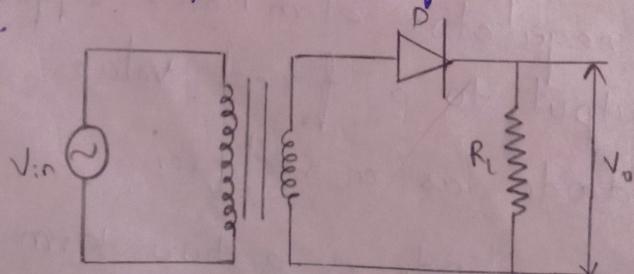The basic half wave rectifier circuit along with its input and output wave forms is shown in below figure



Basic circuit

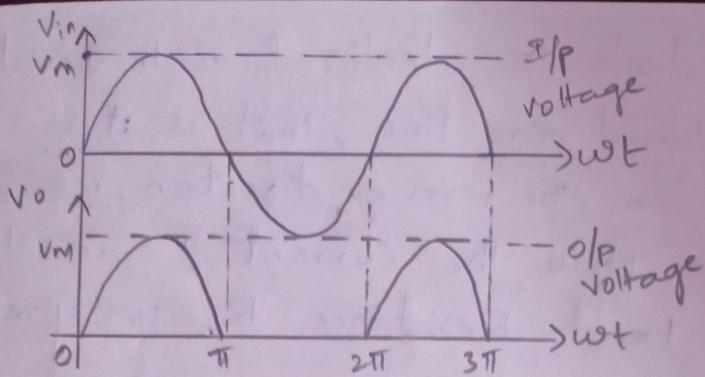

The ac Voltage to be rectified is applied to a single diode connected in series in a load resistor  $R_L$  when it is required to step up or step down the input voltage a power transformer is used.

→ Working of half-wave rectifier:

For the positive half wave rectifier, the input ac voltage the diode 'D' is in forward bias then it conducts. Now the current flows in the circuit and there is a voltage drop across  $R_L$ .

For the negative half cycles of input ac voltage the diode 'D' is in reverse bias then it does not conduct. Now no current flows in the circuit i.e.,  $I_d = 0$  and  $V_d = 0$ . Thus for the negative half cycle no power is delivered to the load.

The output waveforms can be observed with the help of an oscilloscope by connecting it across the load resistor  $R_L$ .

Since Only half-cycles of input wave is used. So it is called as a halfwave rectifier.

Let a sinusoidal voltage ( $V_i$ ) is applied to the input of the rectifier then  $V_i = V_m \sin \omega t$  — ①

where  $V_m$  is the maximum value of supply voltage

Let the diode is idealized with resistance  $R_f$  in the forward direction, That is, it is in 'ON' stage and  $R_f$  is in the reverse direction, i.e; it is in 'OFF' state. Now the current  $I$  in the diode or in the Load Resistance  $R_L$  is given by

$$i = I_m \sin wt \text{ for } 0 \leq wt \leq \pi - \textcircled{2}$$

$$i = 0 \text{ for } \pi \leq wt \leq 2\pi - \textcircled{3}$$

$$\text{where } I_m = \frac{V_m}{R_f + R_L} - \textcircled{4}$$

(i) The dc output current :

Average current  $I_{dc}$  is

$$I_{dc} = \frac{1}{2\pi} \int_0^\pi i d(wt)$$

$$I_{dc} = \frac{1}{2\pi} \left[ \int_0^\pi I_m \sin wt \cdot d(wt) + \int_\pi^{2\pi} 0 \cdot d(wt) \right]$$

$$I_{dc} = \frac{1}{2\pi} \left[ I_m (-\cos wt) \Big|_0^\pi \right] = \frac{1}{2\pi} \left[ I_m (1 - (-1)) \right]$$

$$I_{dc} = \frac{I_m}{\pi} = 0.318 I_m - \textcircled{5}$$

Substituting the value of  $I_m$ ,

$$\text{we get } I_{dc} = \frac{V_m}{\pi(R_f + R_L)} - \textcircled{6}$$

If  $R_L \gg R_f$  then,

$$I_{dc} = \frac{V_m}{\pi R_L} = 0.318 \frac{V_m}{R_L} - \textcircled{7}$$

\* The dc Output Voltage

The d.c Output Voltage is given by

$$V_{dc} = I_{dc} \times R_L = \frac{I_m}{\pi} \times R_L - \textcircled{8}$$

$$= \frac{V_m \times R_L}{\pi(R_f + R_L)} = \frac{V_m}{\pi(1 + \frac{R_f}{R_L})} - \textcircled{9}$$

$$\text{if } R_L \gg R_F \text{ then } V_{dc} = \frac{V_m}{\pi} = 0.318 V_m \quad \rightarrow \textcircled{10}$$

For a half-wave rectifier there is an output voltage for a period from 0 to  $\pi$  and there is no output for the period from  $\pi$  to  $2\pi$ . The Average dc value of Output voltage is given by  $V_{dc} =$

$$V_{dc} = \frac{\text{area of the curve for full cycle}}{\text{base}}$$

$$V_{dc} = \frac{1}{2\pi} \int_0^{2\pi} \frac{V_{id}(wt)}{2\pi} dt = \frac{1}{2\pi} \int_0^{2\pi} V_m \sin wt d(wt)$$

$$V_{dc} = \frac{V_m}{2\pi} [-\cos wt]_0^{\pi} = \frac{V_m}{2\pi} [1 - (-1)]$$

$$V_{dc} = \frac{V_m}{\pi} = 0.318 V_m$$

### (iii) Rms current and Voltage:

The Value of Rms current is given by

$$I_{rms} = \left[ \frac{1}{2\pi} \int_0^{2\pi} i^2 d(wt) \right]^{1/2}$$

$$\therefore I_{rms} = \left[ \frac{1}{2\pi} \int_0^{\pi} I_m^2 \sin^2 wt d(wt) + \frac{1}{2\pi} \int_{\pi}^{2\pi} 0 \cdot d(wt) \right]^{1/2}$$

$$= \left[ \frac{I_m^2}{2\pi} \int_0^{\pi} \left( \frac{1 - \cos 2wt}{2} \right) d(wt) \right]^{1/2}$$

$$= \left[ \frac{I_m^2}{4\pi} \left\{ (wt) - \frac{\sin 2wt}{2} \right\}_0^{\pi} \right]^{1/2}$$

$$= \left[ \frac{I_m^2}{4\pi} \left\{ \pi - 0 - \frac{\sin 2\pi}{2} + \sin 0 \right\} \right]^{1/2} = \left[ \frac{I_m^2}{4} \right]^{1/2}$$

$$I_{rms} = \frac{I_m}{2} \quad \text{--- } \textcircled{11}$$

$$I_{rms} = \frac{V_m}{2(R_F + R_L)} \quad \text{--- } \textcircled{12}$$

Rms voltage across the load is

$$V_{rms} = I_{rms} \times R_L = \frac{V_m \times R_L}{2(R_F + R_L)}$$

$$(Or) \quad V_{rms} = \frac{V_m}{2\left[1 + \frac{R_f}{R_L}\right]} \quad — (13)$$

$$\text{If } R_L \gg R_f \text{ then } V_{rms} = \frac{V_m}{2} \quad — (14)$$

→ Rectifier efficiency:-

The Rectifier efficiency is defined as the ratio of dc output power to the ac input power. It should be represented with  $\eta$  (eta).

$\eta = \frac{\text{dc power delivered to the load}}{\text{ac power input power from secondary transformer}}$

$$\eta = \frac{P_{dc}}{P_{ac}}$$

$$\begin{aligned} \text{Now } P_{dc} &= (I_{dc})^2 \times R_L \\ &= \frac{\pi^2 m \cdot R_L}{T^2} \end{aligned}$$

$$P_{ac} = P_a + P_r$$

$P_a$  = Power dissipated at the Junction of diode

$$P_a = I_{rms}^2 \times R_f \Rightarrow \frac{I_m^2}{4} \times R_f$$

$P_r$  = Power dissipated in the load resistance

$$= I_{rms}^2 \times R_L \Rightarrow \frac{\pi^2 m}{4} \times R_L$$

$$\begin{aligned} \therefore P_{ac} &= \frac{I_m^2}{4} \times R_f + \frac{\pi^2 m}{4} \times R_L \\ &= \frac{I_m^2}{4} (R_f + R_L) \end{aligned}$$

$$\eta = \frac{\frac{\pi^2 m^2 R_L}{T^2}}{\frac{I_m^2 (R_f + R_L)}{4}} = \frac{4}{\pi^2 T^2} \left( \frac{R_L}{R_f + R_L} \right)$$

$$\eta = \frac{0.406}{1 + \frac{R_f}{R_L}}$$

% of rectifier efficiency

$$= \frac{0.406 \times 100}{1 + \frac{R_F}{R_L}} = \frac{40.6}{1 + \frac{R_F}{R_L}} \Rightarrow 40.6\%$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{(I_{dc})^2 R_L}{(I_{rms})^2 R_L} \Rightarrow \frac{(V_{dc} R_L)^2 R_L}{(V_{rms} R_L)^2 R_L} = \frac{V_{dc}^2}{V_{rms}^2}$$

$$\frac{\left(\frac{V_m}{\pi}\right)^2}{\left(\frac{V_m}{2}\right)^2} \text{ (or)} \quad \eta = \frac{4}{\pi^2} = 0.406 = 40.6\%$$

The maximum value of rectifier efficiency of a half wave rectifier is 40.6%, when  $\frac{R_F}{R_L} = 0$

29/7/22  
The Output of a rectifier consists of a dc component as well as ac component. The ac component in the output is called as ripple, more effective will be the rectifier. Thus the ripple factor gives an idea about the rectified voltage and it is defined as the ratio of the effective value of the ac component of Voltage or current to the direct or average value

$$\gamma = \frac{\text{Ripple Voltage}}{\text{dc Voltage}} = \frac{\text{rms Value of ac components}}{\text{dc value of wave}}$$

$$= \frac{(V_r)_{rms}}{V_{dc}} = \frac{V_{ac}}{V_{dc}} = \frac{(\Sigma v)_{rms}}{I_{dc}} = \frac{I_{ac}}{I_{dc}}$$

where  $(V_r)_{rms}$  = rms value of a.c component of output voltage

$V_{dc}$  = d.c value of output voltage

$$\text{Now, } V_{rms}^2 = \sqrt{V_{dc}^2 + (V_r)_{rms}^2} = \sqrt{V_{dc}^2 + V_{ac}^2}$$

$$(V_r)_{rms} = \sqrt{V_{rms}^2 - V_{dc}^2}$$

$$\therefore \gamma = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$

$$\gamma = \frac{\sqrt{\left(\frac{V_m}{2}\right)^2 - \left(\frac{V_m}{\pi}\right)^2}}{\sqrt{\left(\frac{V_m}{2}\right)^2}} - 1 = \sqrt{\left(\frac{\pi}{2}\right)^2 - 1} = 1.21$$

The ripple factor is also defined as  $\gamma = \frac{(\Sigma v)_{rms}}{I_{dc}}$

The effective or rms value of current is given by

$$I_{rms} = \sqrt{I_{dc}^2 + I_1^2 + I_2^2 + I_3^2 + \dots} \Rightarrow \sqrt{I_{dc}^2 + I_{ac}^2} = \sqrt{I_{dc}^2 + (I_r)^2}$$

$$I_{ac} = (I_r)_{rms} = \sqrt{I_1^2 + I_2^2 + I_3^2 + \dots}$$

$$\gamma = \frac{(I_r)_{rms}}{I_{dc}} = \frac{I_{ac}}{I_{dc}} = \sqrt{\frac{I_{rms}^2 - I_{dc}^2}{I_{dc}^2}} = \sqrt{\left(\frac{(I_r)_{rms}}{I_{dc}}\right)^2 - 1}$$

$$\gamma = \sqrt{\frac{(Im/2)^2}{(Im/\pi)^2} - 1} = \sqrt{\frac{(\pi)^2}{2.46} - 1} = 1.21 \quad //$$

→ Voltage Regulation:

It is defined as variation regulation of dc output voltage with change in dc load current.

Thus, percentage of voltage regulation

$$\% \text{ Voltage regulation} = \frac{V_{no\ load} - V_{full\ load}}{V_{full\ load}} \times 100$$

where  $V_{no\ load}$  = Voltage at no load

$V_{full\ load}$  = Voltage at full load.

For an ideal power supply, the output voltage should be independent of the load current. When an ideal power supply has a full load voltage equal to its no load voltage, then it has zero percentage of regulation. However the percentage regulation better would be the power supply.

18/22  
→ Transformer utilization factor:-

The DC power to be delivered to the load in a rectifier circuits decides the rating of the transformer used in the circuits. So, TUF is

$$\begin{aligned} TUF &= \frac{\text{DC power to be delivered to the load}}{\text{AC rating of transformer secondary}} \\ &= \frac{P_{dc}}{P_{ac}(\text{rated})} \end{aligned}$$

According to the theory of transformer the rated voltage of secondary will be  $V_m/\sqrt{2}$  and the actual rms current flowing through it will be  $Im/2$

$$TUF = \frac{(\text{Im}/\pi)^2 \times R_L}{(V_m/\sqrt{2}) (\text{Im}/2)}$$

$$\text{But } V_m = \text{Im} (R_F + R_L)$$

$$\therefore TUF = \frac{(\text{Im}/\pi)^2 \times R_L}{\frac{\text{Im}(R_F + R_L)}{\sqrt{2}} \times \frac{\text{Im}}{2}}$$

$$= \frac{2\sqrt{2}}{\pi^2} \times \frac{R_L}{R_F + R_L}$$

If  $R_L \gg R_F$

$$TUF = \frac{2\sqrt{2}}{\pi^2} = 0.287$$

This mean that if the transformer rating is 1 kVA (1000 VA) then the half wave rectifier can deliver 287 watts to resistance load.

→ Peak inverse voltage (PIN)

We have seen that during negative half cycles in AC input voltage the diode is in reverse bias and does not conducts. Therefore their no current. As a result their is no voltage drop across the load resistance. So, for the negative voltage the input same amount appears as reverse voltage across the diode in the reverse direction. i.e; during non-conducting or off state. Now, we defined the peak inverse voltage as the maximum voltage across the diode in reverse direction.

\* Form factor:

The form factor is defined as

$$F = \frac{\text{rms Value}}{\text{avg value}}$$

$$F = \frac{\text{Im}/2}{\text{Im}/\pi} = \frac{0.5 \text{Im}}{0.314 \text{Im}} = 1.57$$

\* Peak factor

It is defined as  $F = \frac{\text{Peak Value}}{\text{RMS Value}} = \frac{V_m}{V_m/2} = 2$

4/8/22

→ Full wave rectifier :-


Full wave rectifier converts an AC voltage into a pulsating DC voltage by using both half cycles of the applied AC voltage.

It uses two diodes one conducts during one half cycle while the other diode conducts during the other half cycle of the applied AC Voltage.

There are two types of full wave rectifiers.

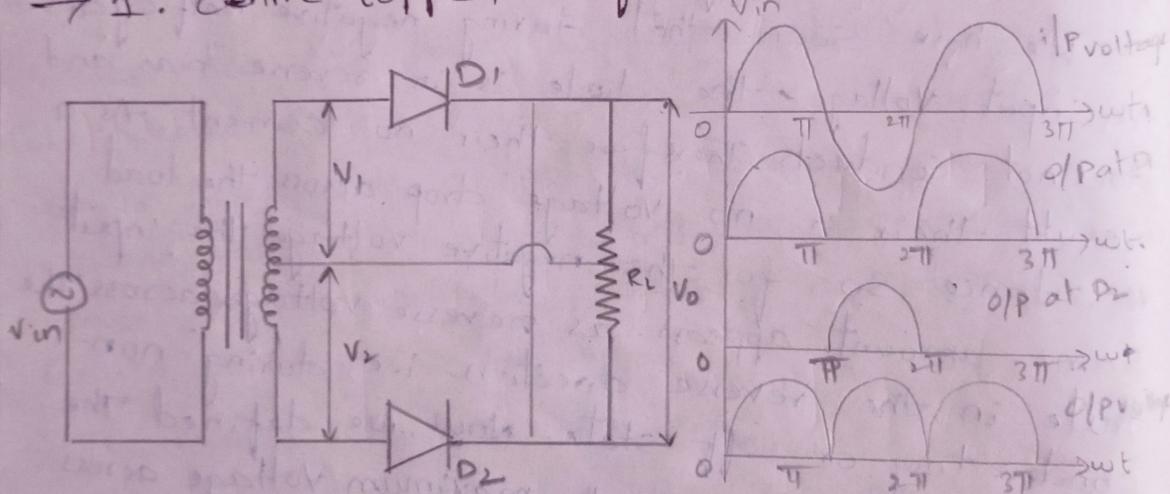1. Centre tapped transformer full wave rectifier
2. Bridge rectifier

→ 1. Centertapped transformer full wave rectifier:



In full wave rectifier both half-cycles of input are utilized with the help of two diodes working alternately. Therefore, in full wave rectifier circuit current flows through load resistors for both direction half-cycles of input AC voltage.

→ Working of full wave rectifier:

During positive half-cycles of AC input voltage, the terminal of the diode \$D\_1\$ is positive and diode \$D\_2\$ is negative.

is negative. Now the diode  $D_1$  is in forward biased i.e; it conducts and causes a current in load resistor  $R_L$  the diode  $D_2$  remains non-conducting with reverse biased.

During negative half-cycles of -Ac input voltage the terminal of diode  $D_2$  becomes positive and the terminal  $D_1$  becomes negative. Now the diode  $D_2$  is in forward biased and it conducts and causes a current  $I$  in load resistor  $R_L$ . Then the diode  $D_1$  remains in non-conducting with reverse biased with reverse biased.

Thus the current flows through  $R_L$  in the same direction in both half-cycles of the Ac input

→ Analysis of full wave rectifier:-

Let the input voltage  $V_i$  is given by

$$V_i = V_m \sin \omega t$$

The current is  $i_1$  through diode  $D_1$  and load resistor  $R_L$  is given by

$$i_1 = I_m \sin \omega t \quad \text{for } 0 \leq \omega t \leq \pi$$

$$i_1 = 0 \quad \text{for } \pi \leq \omega t \leq 2\pi$$

where  $I_m = V_m / R_f + R_L$   $R_f$  being the diode resistance in ON condition.

Similarly the current flowing through  $R_L$  is the diode  $D_2$  and load resistor  $R_L$  is given by

$$i_2 = 0 \quad \text{for } 0 \leq \omega t \leq \pi$$

$$i_2 = I_m \sin \omega t \quad \text{for } \pi \leq \omega t \leq 2\pi$$

The total current flowing through  $R_L$  is the sum of the two current  $i_1$  and  $i_2 \Rightarrow i = i_1 + i_2$

(i) DC or Average Current =

The average value of output current that a dc

ammeter will indicate is given by

$$I_{dc} = \frac{1}{2\pi} \int_0^{2\pi} i_1 d(\omega t) + \int_0^{\pi} i_2 d(\omega t)$$
$$= \frac{1}{2\pi} \int_0^{\pi} I_m \sin(\omega t) d(\omega t) + 0 + 0 + \frac{1}{2\pi} \int_{\pi}^{2\pi} I_m \sin(\omega t) d(\omega t)$$

$$I_{dc} = \frac{I_m}{\pi} + \frac{I_m}{\pi} = \frac{2I_m}{\pi} = 0.636 I_m$$

This is double that of a half-wave rectifier.

(ii) DC output Voltage :-

The dc o/p voltage across load is given by

$$V_{dc} = I_{dc} \times R_L$$
$$= \frac{2I_m}{\pi} R_L = 0.636 I_m R_L$$
$$= \frac{2V_m}{\pi (R_f + R_L)} R_L \text{ if } R_L \gg R_f$$

$$V_{dc} = \frac{2V_m}{\pi} = 0.636 V_m$$

(iii) RMS current :

The RMS value of the current is given by

$$I_{rms} = \left[ \frac{1}{\pi} \int_0^{\pi} i^2 d(\omega t) \right]^{1/2}$$
$$= \left[ \frac{I_m^2}{\pi} \int_0^{\pi} \sin^2(\omega t) d(\omega t) \right]^{1/2} = \frac{I_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

(iv) Rectifier Efficiency :-

The rectifier efficiency is defined by

$$\eta = \frac{P_{dc}}{P_{ac}}$$

$$\text{Now } P_{dc} = (V_{dc})^2 / R_L = \left( \frac{2V_m}{\pi} \right)^2 / R_L$$

$$\text{and } P_{ac} = (V_{rms})^2 / R_L = \left( \frac{V_m}{\sqrt{2}} \right)^2 / R_L$$

$$\eta = \frac{(2V_m/\pi)^2}{(V_m/\sqrt{2})^2} = \frac{8}{\pi^2} = 0.812 = 81.2\%.$$

The dc output power  $P_{dc} = I_{dc}^2 R_L = \frac{4I_m^2 R_L}{\pi^2}$

The ac input power  $P_{ac} = 2I_{rms}^2 (R_f + R_L) = \frac{I_m^2}{2} (R_f + R_L)$

$$\therefore \eta = \frac{4I_m^2 R_L}{\frac{I_m^2}{2} (R_f + R_L)} = \frac{8}{\pi^2} \cdot \frac{R_L}{(R_f + R_L)}$$

$$\text{If } R_L \gg R_f \quad \eta = \frac{8}{\pi^2} = 0.812$$

$$\therefore \eta = 81.2\%$$

Thus, full wave Rectifier has efficiency twice that of half-wave rectifier.

→ Ripple factor :-

The form factor of rectified output voltage of full wave rectifier is given by

$$F = \frac{I_{rms}}{I_{dc}} = \frac{I_m/\sqrt{2}}{2I_m/\pi} = 1.11$$

The ripple factor  $\gamma$  is defined as

$$\gamma = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} = \sqrt{F^2 - 1}$$

$$\gamma = \sqrt{(1.11)^2 - 1} = 0.48$$

\* Voltage Regulation :

The dc output voltage is given by

$$V_{dc} = \frac{2I_m R_L}{\pi} = \frac{2V_m R_L}{\pi(R_f + R_L)} \quad \text{where } R_L \gg R_f \text{ then } R_f \text{ can be neglected.}$$

$$V_{dc} = \frac{2V_m}{\pi}$$

→ Peak inverse voltage :-

PIV is the maximum possible voltage across a diode when it is in reverse biased.

Consider, the diode  $d_1$  is in forward biased i.e; conducting and  $d_2$  is in reverse biased i.e; non conducting. In this case a voltage  $V_m$  is developed across the load resistor  $R_L$ . Now the Voltage across the diode  $d_2$  is the sum of the Voltages across load resistor. Hence PIV of diode  $d_2 = 2V_m$

Similarly PIV of diode  $d_1 = 2V_m$

→ Transformer Utilization factor (TUF):

The <sup>average</sup> TUF in full wave rectifier circuit is determined by considering the primary and secondary winding separately.

$$\begin{aligned} \text{TUF of primary} &= \frac{P_{dc}}{\text{Volt Amp rating of primary}} \\ &= \frac{(I_{dc})^2 R_L}{\left(\frac{V_m}{\sqrt{2}}\right) \left(\frac{2I_m}{\sqrt{2}}\right)} = \frac{\left(\frac{2I_m}{\pi}\right) R_L}{\left(\frac{V_m}{\sqrt{2}}\right) \left(\frac{2I_m}{\sqrt{2}}\right)} \\ &= \frac{4I_m^2}{\pi^2} \cdot \frac{2R_L}{I_m^2(R_f + R_s + R_L)} \end{aligned}$$

where  $R_s$  is the resistance of secondary.


$$\begin{aligned} \text{TUF of primary} &= \frac{8}{\pi^2} \left[ \frac{R_L}{R_f + R_s + R_L} \right] \\ &= \frac{8}{\pi^2} = 0.812 \end{aligned}$$

$$\begin{aligned} \text{But } (\text{TUF})_{avg} &= \frac{P_{dc}}{\sqrt{\text{A rating of Transformer}}} \\ &= \frac{(\text{TUF})_P + (\text{TUF})_S + (\text{TUF})_S}{3} \\ &= \frac{0.812 + 0.287 + 0.287}{3} \end{aligned}$$

$$\boxed{\text{TUF} = 0.693}$$
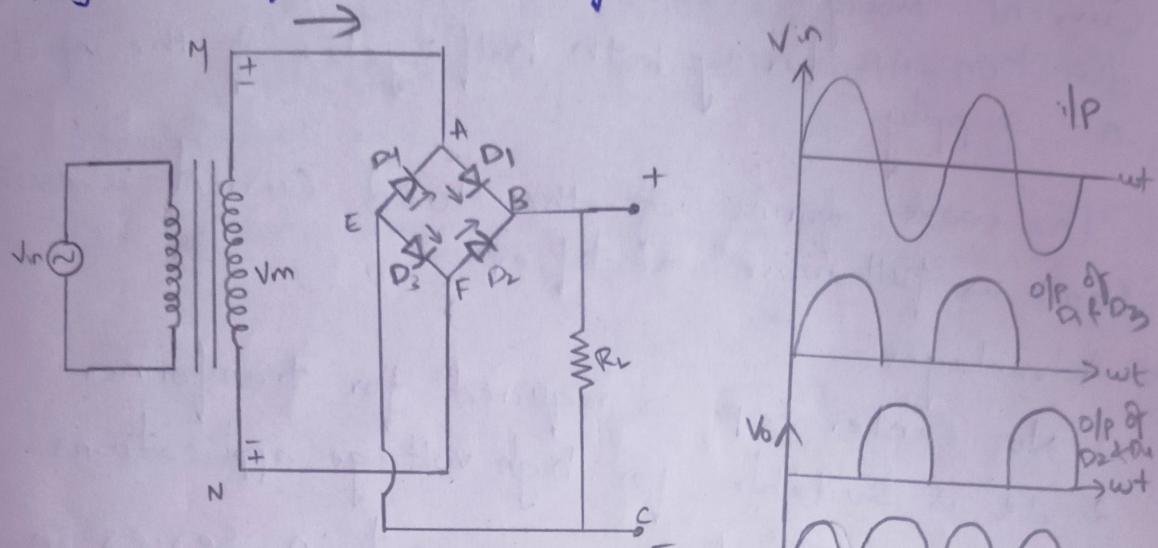
## 5/8/22 Full wave Bridge Rectifier

A circuit frequently used for electronic dc power supply is a full wave bridge rectifier



→ During the half cycles D<sub>1</sub> & D<sub>3</sub> → R.B

→ During -ve half cycles D<sub>2</sub> & D<sub>4</sub> → R.B

10/8/22

In full wave rectifier four diode is used

Here stepdown transformer is used for AC power supply

During the positive input halfcycle the terminal M of the secondary transformer is positive while the terminal N is negative Now the diodes D<sub>1</sub> and D<sub>3</sub> are in forward biased (ON position) i.e; they conduct whereas the diodes D<sub>2</sub> and D<sub>4</sub> are in reverse biased (OFF position) i.e; they do not conduct.

So, a current flows along M-A-B-C-E-F-N their will be a voltage drop across  $R_L$  during the negative input halfcycle the terminal N of the secondary transformer is negative while the terminal M is positive. Now the diodes D<sub>1</sub> and D<sub>3</sub> are in reverse biased (OFF position) i.e; they do not conduct whereas the diodes D<sub>2</sub> and D<sub>4</sub> are in forward biased (ON position) i.e; they do not conduct

So, the current flows along NFBCEAM

It is obvious from the figure that the current through load resistance  $R_L$  in the same direction AB during both half cycles of the input ac supply.

The wave forms of the load current is essentially same as full wave rectifier

\*Advantages:-

1. No center tap is required for transformer.
2. It is suitable for high voltage applications

Since two diodes are present in series in each conduction path the PIV is equally shared by the two diodes. Thus, it has less PIV rating for diodes

→ Analysis:

$$1. I_{dc} = \frac{2Im}{\pi} = 0.636 Im$$

$$2. V_{dc} = \frac{2Vm}{\pi} = 0.636 Vm = 0.636 Im R_L$$

$$3. I_{rms} = \frac{Im}{\pi}$$

$$4. n = \frac{0.812}{(1+R_F/R_L)} \Rightarrow 81.2\% \text{ when } R_F = 0.$$

$$5. \gamma = 0.48$$

6. Peak inverse voltage (PIV)

PIV of a diode in bridge rectifier for positive half cycles of input the diode  $D_1$  and  $D_3$  are in forward bias and  $D_2$  and  $D_4$  are in reverse bias. These diodes have maximum reverse voltage equal to the maximum secondary

voltage ( $V_m$ ). Therefore peak inverse voltage of diode in bridge rectifier is given by  $PIV = V_m$

→ TUF (Transformer utilization factor):

TUF of primary and secondary will be the same as there is always current through primary and secondary

$$\begin{aligned} \text{TUF of secondary} &= \frac{P_{dc}}{\text{N.A rating of Secondary}} \\ &= \frac{I_{av}^2 \cdot R_L}{\left(\frac{V_m}{\sqrt{2}}\right) \left(\frac{I_m}{\sqrt{2}}\right)} \\ &= \frac{(2 \cdot I_m \pi) R_L}{\left(\frac{N_n}{\sqrt{2}}\right) \left(\frac{I_m}{\sqrt{2}}\right)} \\ &= 0.812 // \end{aligned}$$

Hence DC output power is 81.2% of transformer rating

$$\begin{aligned} \text{primary TUF} &= 0.812 \\ \text{TUF}_{ar} &= \frac{(\text{TUF})_p + (\text{TUF})_s}{2} \\ &= \frac{0.812 + 0.812}{2} \end{aligned}$$

$$(\text{TUF})_{average} = 0.812 //$$

A half-wave rectifier supplies power to  $1\text{k}\Omega$  load the input voltage supply is 220 Volts rms neglecting forward resistance ( $r_F$ ) of the diode. Calculate (i)  $V_{dc}$  (ii)  $I_{dc}$  (iii) Ripple Voltage

$$\text{Sol: (i)} V_{dc} = \frac{V_m}{\pi} \Rightarrow \frac{\sqrt{2}V}{\pi} \Rightarrow \frac{\sqrt{2} \times 0.318}{\pi} = \frac{0.45V}{0.14}$$

$$\Rightarrow \sqrt{2}V = \sqrt{2} \times 0.318 = 0.45V$$

$$\Rightarrow 0.45 \times 220V$$

$$V_{dc} = 99V$$

$$(ii) I_{dc} = \frac{V_{dc}}{R_L} = \frac{99V}{1000\Omega} = 99mA$$

$$(iii) V = \frac{V_{rms}}{\sqrt{2}} \Rightarrow V_{rms} = \sqrt{2} \times V_{dc} = 99 \times 1.21 = 119.79V$$

Q. A Sinusoidal voltage of Amplitude 25V and frequency 50Hz is applied to a half wave rectifier using PN diode. No filter is used and the load resistance is 1000(ohm.s). The forward resistance of ideal diode is 10Ω. calculate values of load current

(i) Peak, Average, Rms values of load current

(ii) DC power Output

(iii) AC power input

(iv) Rectifier efficiency

(v) Ripple factor

$$\text{soln} (i) I_m = \frac{V_m}{R_f + R_L} = \frac{25}{10 + 1000} = \frac{25}{1010} = 24.7mA$$

$$I_{dc} = \frac{I_m}{\pi} = \frac{24.7}{\pi} = 7.86mA$$

$$I_{rms} = \frac{I_m}{2} = \frac{24.7}{2} = 12.35mA$$

$$(ii) P_{dc} = (I_{dc})^2 R_L \\ = (7.86 \times 10^{-3})^2 \times 1000\Omega$$

$$= (7.86)^2 \times 10^{-6} \times 1000\Omega \\ = 61.77 \times 10^{-3} = 61.77mW$$

$$(iii) P_{ac} = (I_{rms})^2 [R_f + R_L] \\ = (12.35 \times 10^{-3})^2 [10 + 1000] \\ = (12.35 \times 10^{-6})(1010) \\ = 154mW$$

$$(iv) \eta = \frac{P_{dc}}{P_{ac}} \times 100 = \frac{61.77}{154} \times 100 = 40.11$$

$$(v) r = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} = \sqrt{\left(\frac{12.35}{7.86}\right)^2 - 1} = 1.21$$

Q. - AC voltage of 230V applied to a half-wave rectifier circuit through a transformer of turn ratio 10:1. The load resistance value is  $1\text{k}\Omega$  and diode internal resistance is  $20\text{\Omega}$ . Calculate (i)  $I_m$ ,  $I_{dc}$ ,  $I_{rms}$  (ii) DC power output (iii) AC power input (iv) Rectifier efficiency (v) DC Output Voltage (vi) PIV (Peak inverse voltage).

The rms value of voltage applied to the rectified circuit is given by  $V_{rms} = \frac{N_2}{N_1} \times V_{in} = \frac{1}{10} \times 230\text{V} = 23\text{V}$

$$V_m = \sqrt{2} V_{rms} = \sqrt{2} \times 23 = 32.53\text{V}$$

$$(i) I_m = \frac{V_m}{R_f + R_L} = \frac{32.53}{20 + 1000} = 31.89\text{mA}$$

$$I_{dc} = \frac{I_m}{\pi} = \frac{31.89}{\pi} = 10.15\text{mA}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{31.89}{\sqrt{2}} = 15.945\text{mA}$$

$$(ii) P_{dc} = (I_{dc}^2) R_L = (10.15)^2 1000 \times (10^{-3})^2 \\ = 103.02 \times 10^{-3} \\ = 103.02\text{mW}$$

$$(iii) P_{ac} = (I_{rms}^2)[R_f + R_L] \\ = (15.945)^2 \times (10^{-3})^2 [20 + 1000] \\ = 254.24 \times 1020 \times 10^{-6} \\ = 259324.8 \times 10^{-6} = 259.3248 \times 10^{-3} \\ = 259.3248\text{mW}$$

$$(iv) \eta = \frac{P_{dc}}{P_{ac}} \times 100 = \frac{103.02}{259.3} \times 100 = 0.397 \times 100 = 39.7$$

$$(v) V_{dc} = I_{dc} \times R_L = 10.15 \times 1000 \times 10^{-3} = 10150 \times 10^{-3} \text{V} \\ = 10.15\text{V}$$

(vi) PIV of half-wave rectifier is  $V_m = 32.53\text{V}$

Q. A full wave rectifier supplies a load  $1\text{k}\Omega$ . The AC voltage applied to the diodes is  $220\text{V}_{rms}$  if diode resistance is neglected. Calculate 1. Average dc voltage

2. Average dc current ( $I_{dc}$ )

3. Ripple Voltage (rms)

$$\text{Sol: } (i) V_{dc} = \frac{2V_m}{\pi}$$

$$V = \frac{V_m}{\sqrt{2}}$$

$$V_m = V(\sqrt{2})$$

$$V_m = 0.636 V_m = 0.636 \times 220 \times \sqrt{2}$$

$$V_{dc} = 198V$$

$$(ii) I_{dc} = \frac{V_{dc}}{R_L} = \frac{198}{1000} = 198 \text{ mA}$$

$$(iii) \gamma = \frac{V_r(\text{rms})}{V_{dc}} \times 100$$

Q. A full wave P-N diode rectifier uses load resistor of  $1500\Omega$  no filter is used. Assume each diode have idealized characteristic with  $R_f = 10\Omega$  and  $R_s = \infty$ . Since wave voltage applied to each diode has amplitude of  $\approx 30V$  and frequency  $50\text{Hz}$ . calculate  
(i) Peak, dc and rms load current  
(ii) DC power output  
(iii) AC power input  
(iv) Rectifier efficiency

$$\text{Sol: Given } V_m = 30V, R_L = 1500\Omega$$

$$R_f = 10$$

$$(i) I_m = \frac{V_m}{R_f + R_L} = \frac{30}{1500 + 10} = \frac{30}{1510} = 0.01986 \text{ A}$$

$$I_{dc} = \frac{2I_m}{\pi} = \frac{2(19.8 \times 10^{-3})}{3.14} = 19.8 \text{ mA}$$

$$= \frac{39.6}{3.14} = 12.611 \text{ mA}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{19.8}{\sqrt{2}} = 14 \text{ mA}$$

$$\begin{aligned}
 \text{(ii)} \quad P_{dc} &= (I_{dc}^2) R_L = (12.61)^2 (10^3)^2 \times 1500 \\
 &= 159.01 \times 1.5 \times 10^{-3} \\
 &= 238.515 \times 10^{-3} = 238.5 \text{ mW.}
 \end{aligned}$$

$$\begin{aligned}
 \text{(iii)} \quad P_{ac} &= I_{rms}^2 (R_f + R_L) \\
 &= (14 \times 10^{-3})^2 (10 + 1500) = 196 (10^{-6}) (1510) \\
 &= 295960 \times 10^{-6} = 295.9 \times 10^{-3} \text{ mW.}
 \end{aligned}$$

$$\text{(iv)} \quad \eta = \frac{P_{dc} \times 100}{P_{ac}} = \frac{238.5}{295.9} \times 100 = 0.806 \times 100 = 80.6\%.$$


11/8/22:  
Q. In the centre tap circuit shown in below figure calculate

- i) Average current      ii) DC Output Voltage (V<sub>DC</sub>)
- iii) DC output power    iv) AC input power

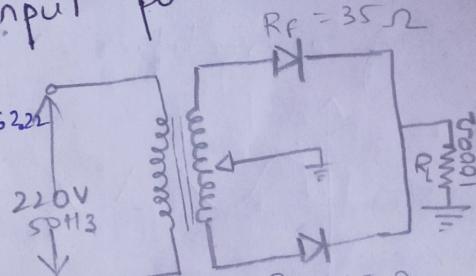v) Rectifier efficiency  
i)  $V_{rms} = 220 \times \frac{N_2}{N_1} = 120 \times \frac{1}{2} = 44V$  &  $V_m = 62.22$   
Maximum voltage across

Secondary winding

$$= \frac{V_m}{2} = \frac{62.22}{2} = 31.11$$



$$I_{dc} = \frac{2 I_m}{\pi} = 19.14 \times 10^{-3} \times 1000 = 19.14 \text{ Volts}$$

$$\text{ii) } V_{dc} = I_{dc}^2 \times R_L = (19.14 \times 10^{-3})^2 \times 1000 \\ = 366.33 \text{ mA}$$

$$\begin{aligned}
 P_{ac} &= I_{rms}^2 (R_f + R_L) = \left( \frac{I_m}{\sqrt{2}} \right)^2 (R_f + R_L) \\
 &= \frac{I_m^2}{2} (R_f + R_L) = \frac{V_m^2}{2(R_f + R_L)} \times (R_f + R_L) \\
 &= \frac{V_m^2}{2(R_f + R_L)}
 \end{aligned}$$

$$P_{ac} = \frac{(V_m)^2}{(R_f + R_L)^2} \times 2(R_f + R_L) = P_{ac} = 467.5 \text{ mW} //$$

v) Rectifier

$$\eta = \frac{P_{dc}}{P_{ac}} \times 100$$

$$= \frac{366.33}{467.5} \times 100$$


$$\eta = 78.4\%$$

$$\text{efficiency} = 78.4\%$$

filter :-



The Output of a rectifier is pulsating i.e.; it has DC value and some AC variations known as ripples.

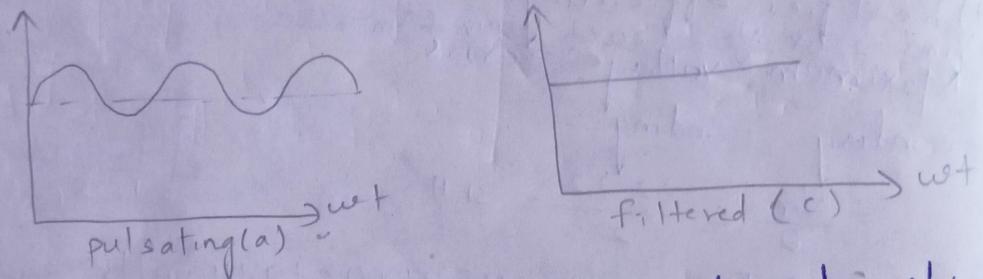- \* In most of the electronic circuits or devices a very studied DC output is required.
- \* This is achieved with the help of a device known as filter
- \* Thus a device that converts the pulsating output of a rectifier into a steady DC level.



- \* The filter circuits are commonly classified as 1) series inductor filter 2) shunt capacitor filter 3) LC filter 4) CLL filter or  $\pi$  filter

### 1. Series Inductor filter

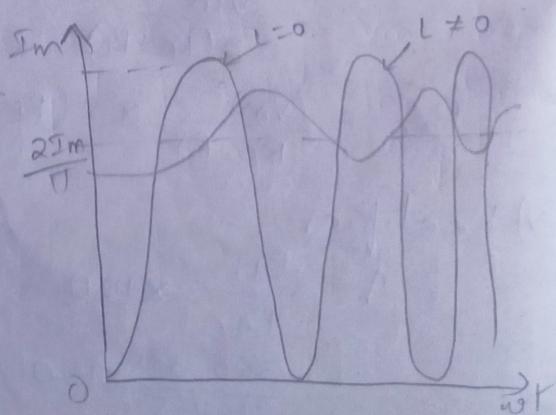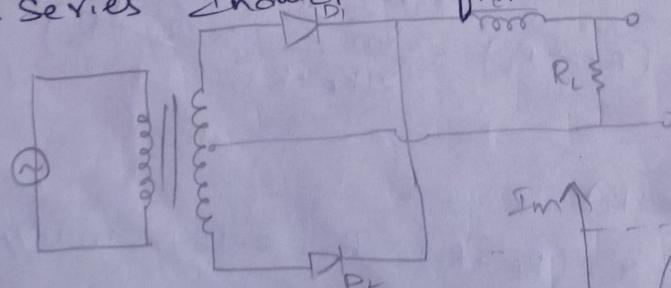

A full wave rectifier with series inductor shown in above figure. The inductor is in series with the load ~~so~~ serves as a filter

The inductor offers high impedance to AC variations since the dc resistance of large inductance is very small. This action is based on the property of inductance to oppose any change of current that may flow through it.

Therefore, AC component of rectifier output is blocked while the dc component reaches at the load.

Theoretically the output should contain dc voltage, but practically it contains a small AC component as well. The above waveform shows the load current with and without filter.

When the output current of the rectifier increases, above a certain average value magnetic energy is stored in the inductor.

17/8/22  
The current flowing in a full wave rectifier without filter is given by

$$i = \frac{2Im}{\pi} - \frac{4Im}{\pi} \sum_{k=2}^{\infty} \frac{\cos kwt}{(k-1)(k+1)}$$

$$i = \frac{2Im}{\pi} - \frac{4Im}{3\pi} \cos 2wt - \frac{4Im}{15\pi} \cos 4wt$$



$$\therefore i = \frac{2Im}{\pi} - \frac{4Im}{3\pi} \cos 2wt //$$

→ Ripple factor:-

The ripple factor is defined as the ratio of rms value of the ac component to the dc value of the wave. i.e;  $\gamma = \frac{(Ir)_{rms}}{I_{dc}}$

The inductor filter should be used when load resistance is small then effective filtering takes place if load current is high  
 → Shunt Capacitor filter :-

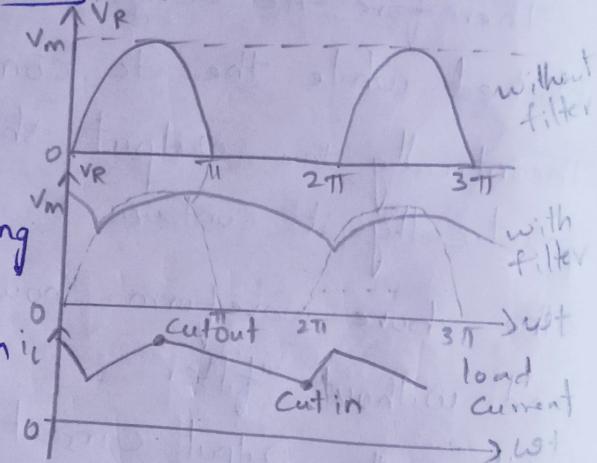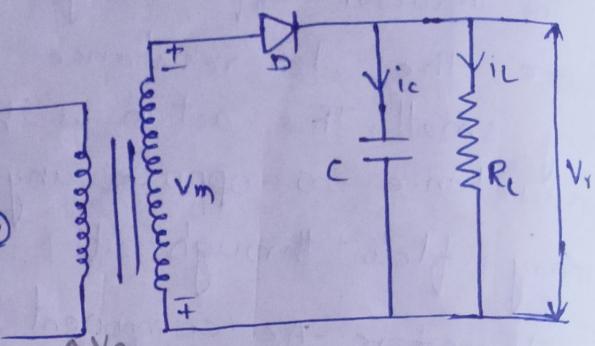The output of a rectifier is pulsating in nature. That is it contains a large no. of ripple components. These ripple components are filtered by putting a filter circuit with the full rectifier of load. Filtering is frequently done by shunting the capacitor with load. This type of filter is known as capacitor input filter



The action of the filter circuit is depend upon the fact that a capacitor stores energy when conducting (charging) and delivers this energy to the load during non-conduction (Discharging). Through this process the ripple components are reduced

During positive half cycles of ac input, the diode is in forward bias then it conducts and the capacitor quickly charges to a voltage  $V_m$ . When the capacitor is fully charged, it holds the charge till input ac supply to the rectifier goes negative


During negative half cycles of ac input, the diode is in reverse bias that is, it does not conduct, so the capacitor discharge through the load resistor.

Usually the discharging time is 100 times more than the charging time. Hence the capacitor does not have sufficient time to discharge appreciably. Due to this the voltage decreases slightly.

By considering the diode current it is significant to know over what portion of the complete cycle is the diode conducting. Complete cycle at which the conduction start is the instant at which the conduction starts is called the cut-in point.

The instant at which the conduction stops is called the cut-out point.

→ L-C filter (or) choke input filter:

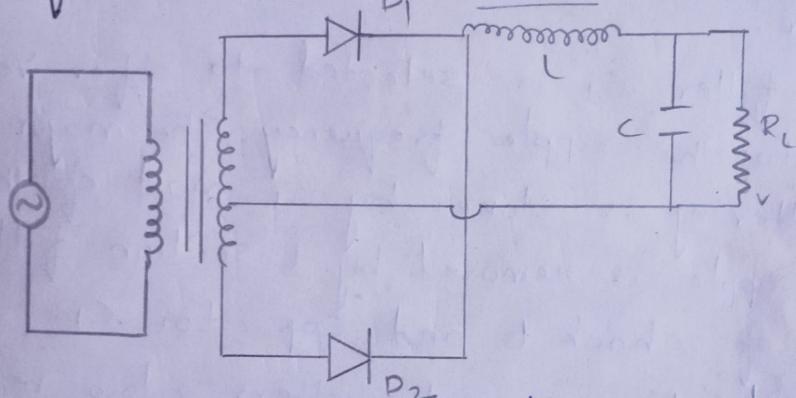

In inductor filter the ripple factor is directly proportional to the load resistance while in capacitor filter inversely proportional to load resistance. Therefore the capacitor has low ripple at heavy loads while inductor filter has small loads.

The combination of these two filters may be selected to make the ripple independent of load resistances.

The resultant filter is called as choke input filter (or) L-C filter

The capacitor is connected in shunt with the load and it offers very low reactance. On the other hand the inductor offers high impedance due to

the combination of both capacitor and inductor.  
Most of the ripple voltage is eliminated from the load voltage

→ CLC filter (or) PI( $\pi$ ) filter:-


A very smooth output may be obtained by a filter consisting of one inductance and two capacitance connected across its each end as these components are arranged in the form of PI( $\pi$ ). So this filter is called as PI( $\pi$ ) filter.

In this filter  $C_1$  is selected to offer very low reactance to the ripple frequency. The major part of the filtering is done by  $C_1$ , most of the remaining ripple is removed by L section filter consisting of choke L and capacitor  $C_2$ .

→ Capacitor  $C_1$ :  
We know that a capacitor offers a low reactance path to ac component of rectifier output while it offers infinite resistance to dc component. Therefore the capacitor  $C_1$  bypasses the amount of ac component to ground and the dc component to pass through it.

Inductor L :-

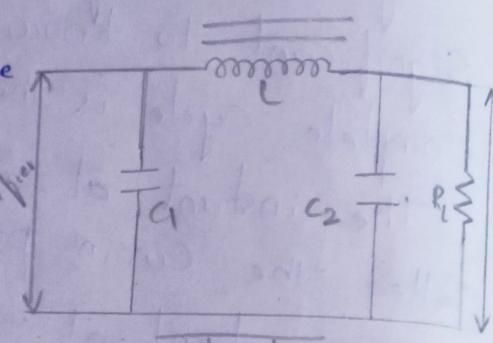We know that an inductor offers a high reactance to ac component of rectifier output while zero resistance to dc component as a result it allows the dc component to pass through it and blocks the ac component which could not be bypassed by capacitor  $C_1$ .



Capacitor  $C_2$ :

If further bypasses the ac component of rectifier output which could not be blocked by an inductor  $L$

From fourier series analysis, of the waveform

$$V = V_{dc} - \frac{N_{max}}{\pi} \left[ \sin 2\omega t - \frac{\sin 4\omega t}{2} + \frac{\sin 6\omega t}{3} + \dots \right]$$

$$\text{But } V_{rms} = \frac{T_{dc}}{2fc} \quad (v_r)_{rms}$$

The second harmonic RMS value is

$$V_2' = \frac{V_{rms}}{\pi\sqrt{2}} = \frac{I_{dc}}{2\sqrt{2}\pi fc}$$

$$V_2' = \frac{I_{dc}}{\sqrt{2}(2\pi fc)} \times \frac{2}{2} = \sqrt{2} I_{dc} X_C$$

$$\text{where } I_{dc} = \frac{V_{dc}}{R_L}$$

$$V_2' = \sqrt{2} \left( \frac{V_{dc}}{R_L} \right) X_C$$

$V_2'$  is applied to the L-section ( $L_1, C_1$ ) by using the same logic the o/p ripple is

$$V_2' \left( \frac{X_{C_1}}{X_{L_1}} \right)$$

$$V_{r_{rms}} = V_2' \left( \frac{X_{C_1}}{X_{L_1}} \right)$$

$$V_{r_{rms}} = \sqrt{2} V_{dc} \left( \frac{X_C}{R_L} \right) \left( \frac{X_{C_1}}{X_{L_1}} \right)$$

$$r = \frac{V_{r_{rms}}}{V_{dc}} = \sqrt{2} \left( \frac{X_C}{R_L} \right) \left( \frac{X_{C_1}}{X_{L_1}} \right)$$