

$$C$$

$$V = \frac{1}{C} \int I \cdot dt$$

$$\dot{Q} = C \cdot \frac{dV}{dt}$$

$$P = CV \cdot \frac{dV}{dt}$$

$$\omega = \frac{1}{2} CV^2$$

$$\dot{I}_3 = \frac{V}{3} = 10$$

KCL (Kirchoff's Current Law):

KCL states that the sum of currents entering into the node is equal to the sum of the currents leaving from that node.


(or).

The algebraic sum of all the currents at a particular node or junction is equal to zero.

$$\dot{I} = 0$$

Current division

$$\dot{I}_T =$$

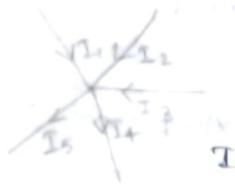


$$I_1 + I_2 + I_3 = I_4 + I_5$$

$$I_1 + I_2 + I_3 - I_4 - I_5 = 0.$$

Ex:-

20A

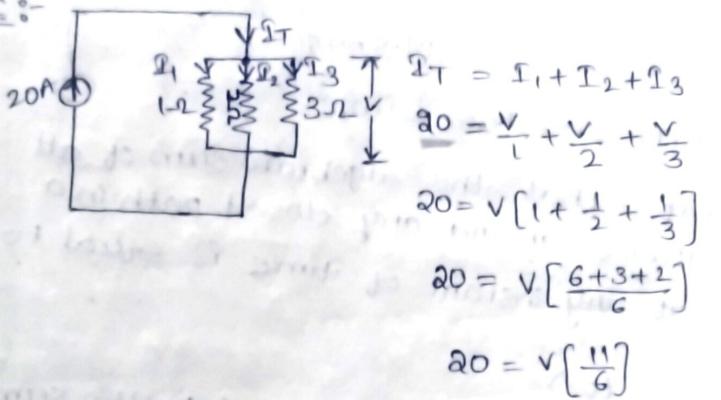

$$20 = \frac{V}{1} + \frac{V}{2} + \frac{V}{3}$$

$$20 = V \left[1 + \frac{1}{2} + \frac{1}{3} \right]$$

$$20 = V \left[\frac{6+3+2}{6} \right]$$

$$20 = V \left[\frac{11}{6} \right]$$

$$V = \frac{20 \times 6}{11} = \frac{120}{11} = 10.9 \text{ Volts}$$

$$I_1 = \frac{V}{1} = \frac{10.9}{1} = 10.9 \text{ Amp}$$

$$I_2 = \frac{V}{2} = \frac{10.9}{2} = 5.45 \text{ Amp}$$

$$I_3 = \frac{V}{3} = \frac{10.9}{3} = 3.63 \text{ Amp}$$

$$I_1 + I_2 + I_3 = 10.9 + 5.45 + 3.63 \\ = 19.98 \text{ Amp}$$

$$IT \approx I_1 + I_2 + I_3$$

Current division rule :-

$I = \frac{\text{opposite resistance}}{\text{total resistance}} \times \text{total current}$

$$I_1 = \frac{2/13}{(2/13)+1} \times 20 = \frac{\left(\frac{2 \times 3}{2+3}\right)}{\left(\frac{2 \times 3}{2+3}\right)+1} \times 20 \\ = 10.9 \text{ AMP.}$$

$$I_2 = \frac{(1/13)}{(4/13)+2} \times 20 = 5.4 \text{ Amp}$$

10.9
 5.4
 3.6
19.9

$$I_3 = \frac{(1/12)}{(1/12)+2} \times 20 = 3.6 \text{ Amp}$$

$$I_T = I_1 + I_2 + I_3 = 10.9 + 5.4 + 3.6 \\ = 19.9 \text{ Amp}$$


KVL (Kirchoff's Voltage Law) :-

KVL states that the algebraic sum of all branch voltages around any closed path in a circuit at any instant of time is equal to zero.

(or)

The total voltage is equal to the sum of voltage drops at individual resistance elements. KVL is also called as conservation of energy.

Ex:-

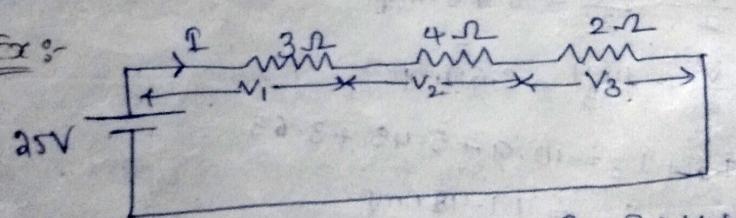

$$R = 3 + 4 + 2$$

$$V_T = V_1 + V_2 + V_3 = 9 \Omega$$

$$V_T = IR = 2.77 \text{ Amp} \quad I = \frac{V}{R}$$

$$V_1 = IR_1$$

$$I = \frac{25}{9} = 2.77 \text{ Amp}$$

$$V_2 = IR_2$$

$$V_3 = IR_3$$

10.9
5.4
3.6
19.9

$$V_1 = 2 \cdot 77 \times 3$$

$$\Rightarrow 8.81 = 8.31 V$$

$$V_2 = 2 \cdot 77 \times 4$$

$$\Rightarrow 11.08 = 11.08 V$$

$$V_3 = 2 \cdot 77 \times 2$$

$$\Rightarrow 5.54 = 5.54 V$$

$$\begin{array}{r} 2.7 \\ \hline 5.4 \\ \hline 8.1 \end{array}$$

$$\begin{array}{r} 2.7 \\ \hline 4 \\ \hline 10.8 \end{array}$$

$$V_T = V_1 + V_2 + V_3$$

$$= 8.31 + 11.08 + 5.54$$

$$= 24.93$$

$$25 \approx 24.93$$

of
ents.

By using voltage division rule :-

$$\frac{\text{Same resistance}}{\text{total resistance}} \times \text{total voltage.}$$

$$V_1 = \frac{3}{93} \times 25 = 8.33 V$$

$$V_2 = \frac{4}{9} \times 25 = 11.11 V$$

$$V_3 = \frac{2}{9} \times 25 = 5.55 V$$

$$V_T = V_1 + V_2 + V_3 = 24.99$$

$$25 \approx 24.99$$

iii) Linear and non-linear


iv) Lumped and distributed.

i) Active and passive :-


Energy sources (V and \mathfrak{I}) are active elements capable of delivering power to some external device.

Passive elements are those which are capable only of receiving power. Inductors and capacitors are capable of storing a finite amount of energy and return it later to an external element.

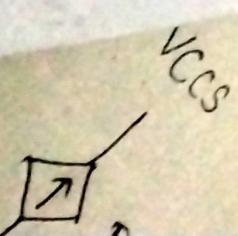and
current
with
ii) Bilateral and Unilateral :-
voltage current flowing in




KLO

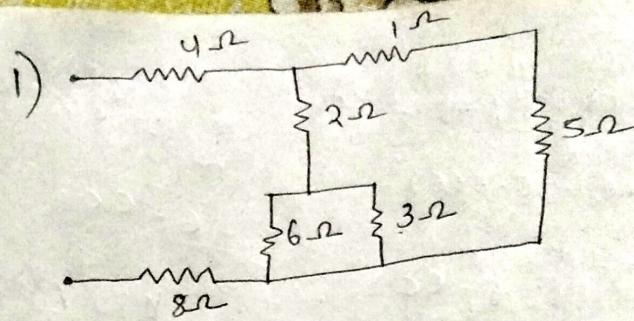

$$P = \frac{V^2}{R}$$


$$P = \frac{V^2}{2R}$$
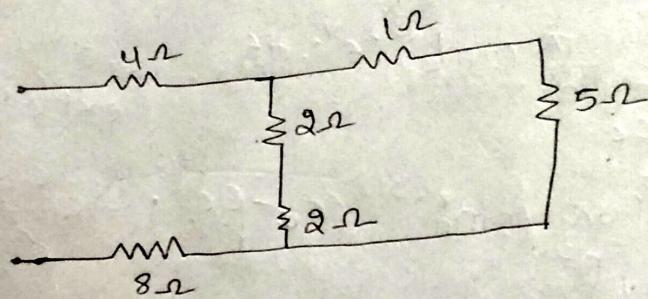
$$Req_1 = \frac{6 \times 3}{6+3} = \frac{18}{9} = 2\Omega.$$




$$Req_2 = 2 + 2 = 4\Omega$$

$$Req_3 = 5 + 1 = 6\Omega$$

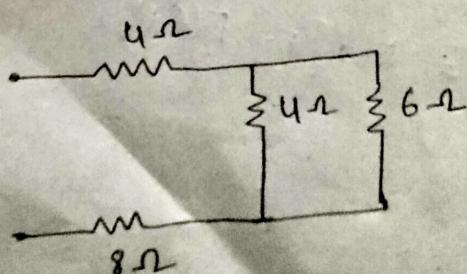

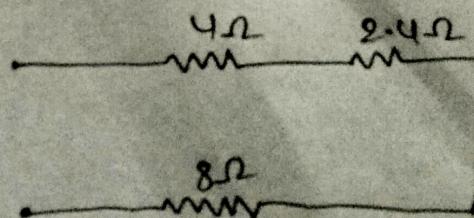
$$Req_4 = \frac{4 \times 6}{4+6} = \frac{24}{10} = 2.4\Omega$$



$$R_{eq\ 5} = 4 + 2 \cdot 4 + 8 \\ = 14.4 \Omega$$

$\therefore R_{eq} = 14.4 \Omega$

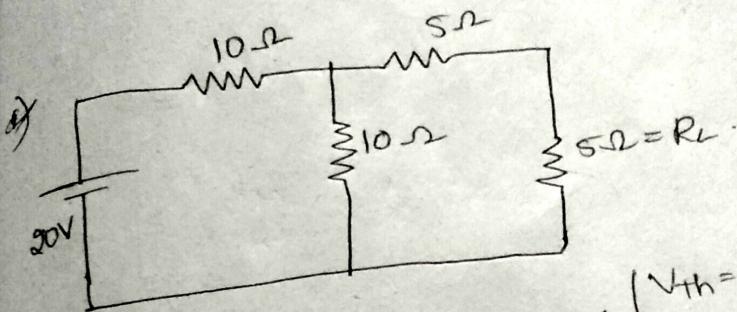


$$V_{th} = \frac{10}{20} \times 20 = 10V \quad (V_{th} = \frac{10}{10+10} \times 20)$$

$$R_{th} = (10//10) + 5 \quad (R_{th} = (10//10) + 5).$$


$$= \frac{100}{20} + 5 \quad (Q = \frac{V_{th}}{R_{th} + R_L}) \\ = 10 \Omega$$

$$I = \frac{10}{10+5} = \frac{10}{15} = 0.66 \text{ Amp}$$

(Mesh Analysis:-)

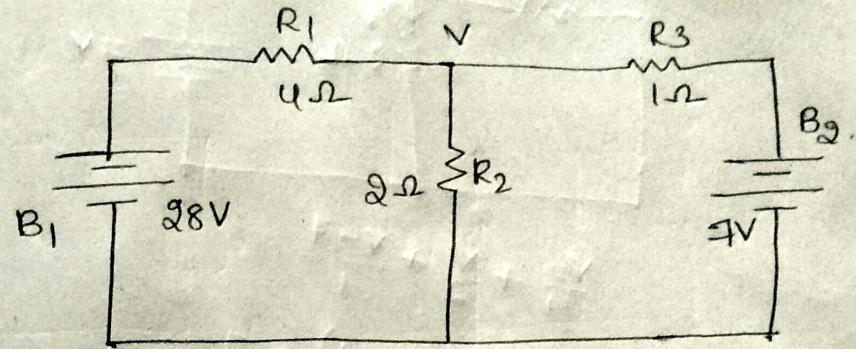

case(i):

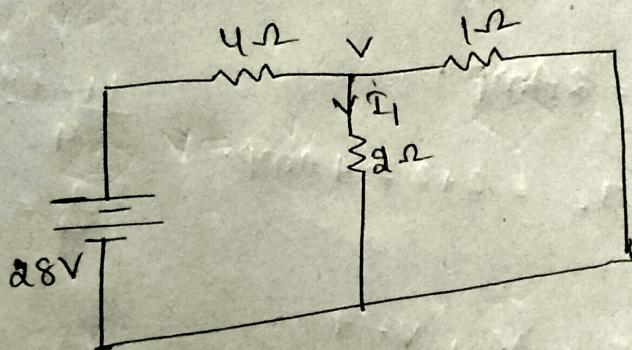

$$= \frac{v-28}{4} + \frac{v}{8} + \frac{v}{1}$$

$$= \sqrt{\left(\frac{1}{a} + \frac{1}{b} + 1\right)} = 7$$

$$= \sqrt{[0.25 + 0.5 + 1]} = 7$$

$$\Rightarrow \sqrt{1.75} = 7$$

$$V = \frac{4}{1.75} = 4$$

$$I_1 = \frac{4}{2} = 2 \text{ Amp}$$

$$\frac{1}{4} + \frac{1}{2}$$

$$\frac{2+4}{8}$$

$$\frac{2+4}{8} = \frac{6}{8} + 1 = 6 + \frac{1}{8}$$


$$\frac{6}{8} + 1 = \Sigma$$

$$\frac{6+8}{8} = \frac{14}{8}$$

$$\frac{14}{8} = 7$$

$$\frac{7 \times 8}{\sqrt{4}}^4$$

Case (ii) :-

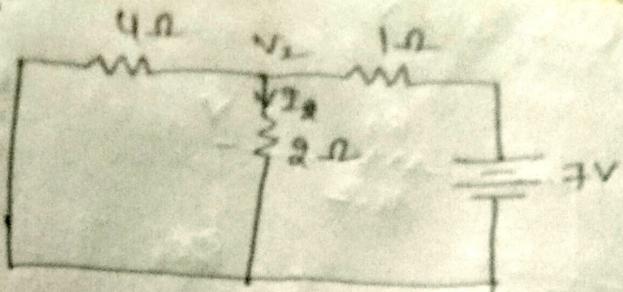

$$\frac{V_2}{4} + \frac{V}{2} + \frac{V-7}{1}$$

$$\sqrt{\left(\frac{1}{4} + \frac{1}{2} + 1\right)} = 7$$

$$V = 4$$

$$I_2 = \frac{4}{2} = 2 \text{ Amp}$$

$$I = I_1 + I_2 = 2 + 2 = 4 \text{ Amp}$$

$$\frac{1+2+4}{4}$$

$$\frac{1}{4} = 1$$

Case (iii) :-

$$\frac{V-28}{4} + \frac{V}{2} + V-7$$

$$\sqrt{\left(\frac{1}{4} + \frac{1}{2} + 1\right)} = 14$$

$$\sqrt{\left(\frac{14}{8}\right)} = 14$$

$$V = 8$$

$$\frac{84}{8}$$

$$20V$$


$$\frac{V}{2} = 0.25V \text{ across } 2\Omega$$

$$2\text{V} = 5A \times 2\Omega + 10A = 20V$$


$$V = IR \Rightarrow V = 20 \times 0.25 = 5V$$

~~(No analysis)~~

~~No Analysis~~

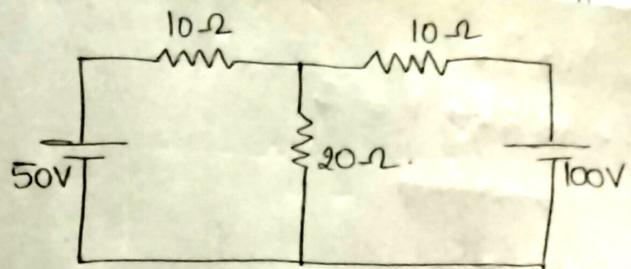

case(i) :-

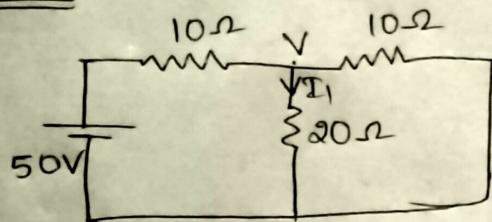

$$\frac{V-50}{10} + \frac{V}{20} + \frac{V}{10}$$

$$\sqrt{\left(\frac{1}{10} + \frac{1}{20} + \frac{1}{10}\right)} = 5$$

$$\sqrt{0.1 + 0.05 + 0.1} = 5$$

$$\sqrt{0.25} = 5 \Rightarrow V = \frac{5}{0.25} = 20$$

$$I_1 = \frac{20}{20} = 1 \text{ Amp.}$$

case (ii) :-

$$\frac{V}{10} + \frac{V}{20} + \frac{V-100}{10}$$

$$\sqrt{\left(\frac{1}{10} + \frac{1}{10} + \frac{1}{20}\right)} = 10 \quad I_2 = \frac{40}{20}$$

$$\sqrt{0.25} = 10 \Rightarrow 40 \quad I_2 = 20 \text{ Amp.}$$



$$I = I_1 + I_2$$

$$= 10 \cdot 2 + 1 = 3$$

~~3 Amp.~~

$$I = 3 \text{ Amp}$$

problem 1

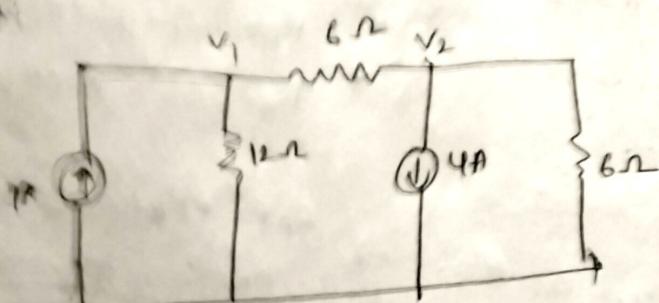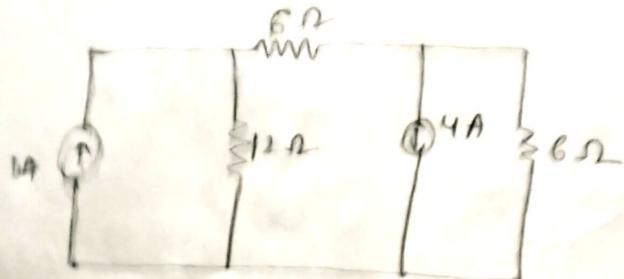

for node 1 :- $-1 + \frac{V_1}{12} + \frac{V_1 - V_2}{6} = 0$

$$-12 + V_1 + 2V_1 - 2V_2 = 0$$

$$3V_1 - 2V_2 = 12 \quad \textcircled{1}$$

for node 2 :- $4 + \frac{V_2 - V_1}{6} + \frac{V_2}{6} = 0$

$$24 + V_2 - V_1 + V_2 = 0$$

$$24 + 2V_2 - V_1 = 0$$


$$V_1 - 2V_2 = 24 \quad \textcircled{2}$$

by solving eq's $\textcircled{1} + \textcircled{2}$

$$V_1 = -6V, V_2 = 18V$$


$$V_g = -15V$$

problem :-

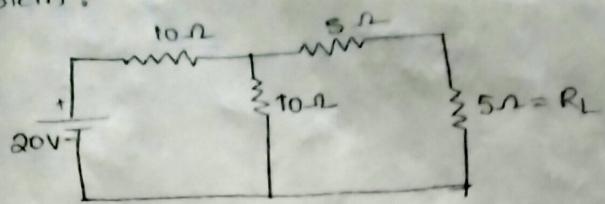


Thevenin's Theorem.

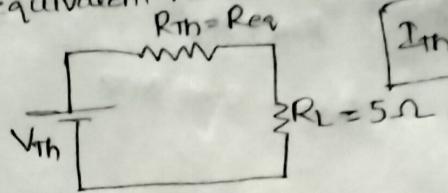For \rightarrow equivalent resistance is -




$$R_{th} = R_{eq}$$

$$I_{th} = \frac{V_{th}}{R_{th} + R_L}$$

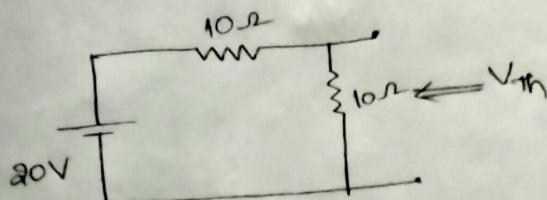
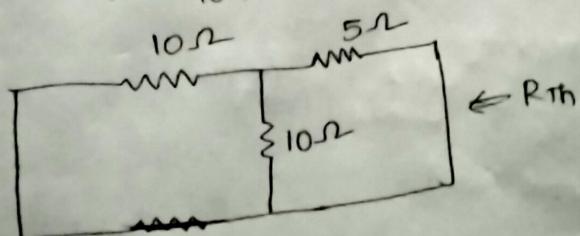
$$V_{th} = \frac{10}{10+10} \times 20 = \frac{10}{20} \times 20 = 10 \text{ Volts}$$




$$R_{th} = (10//10) + 5$$

$$= \frac{10 \times 10}{10+10} + 5$$

$$= \frac{100}{20} + 5$$

$$R_{th} = 5 + 5 = 10 \Omega$$

equivalent resistance R_{th} -

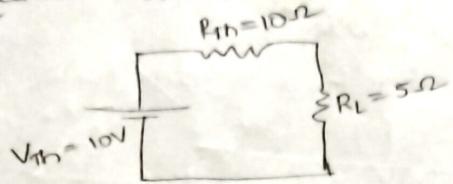

$$V_{th} = 10$$

$$R_{th} = 10$$

$$R_L = 5$$

$$\frac{10}{20} = 0.5$$

$$I_{th} = \frac{V_{th}}{R_{th} + R_L} = \frac{10}{10 + 5} = \frac{10}{15} = 0.66 \text{ Amp}$$

$$I_{th} = 0.66 \text{ Amp}$$

BITS :-

1) B

V_{th}

2) D

3) C

4) A

5) C

6) ~~zero infinity~~

$$7) \frac{1}{L_1} + \frac{1}{L_2} = \frac{L_1 L_2}{L_1 + L_2} = \frac{1}{L_{eq}}$$

8) magnetic field

9) Farad

- 10) power calculation.

11) A

12) C

13) A

14) B

$$I_{th} = 10$$

$$R_{th} = 15$$

$$R_L = 5$$

$$\frac{10}{20} = 0.5$$

$$\frac{10}{15} = 0.66$$

Amp

15) C

16) electrical field

17) power calculation

18) Henry

19) short circuit

20) Linear bilateral Network