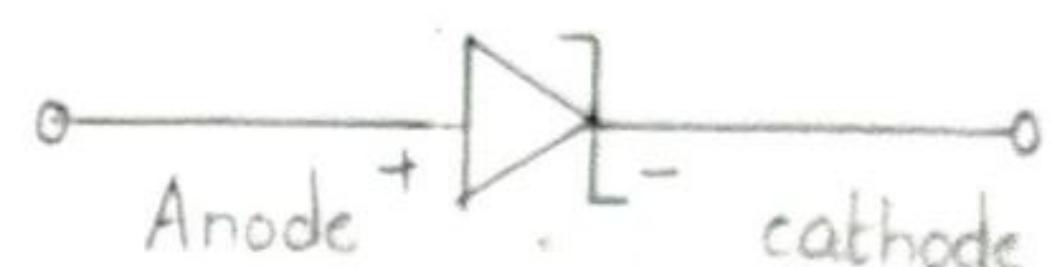


ZENER DIODE CHARACTERISTICS:-


Zener diode is a reverse biased heavily-doped silicon (or germanium) p-n junction diode which is operated in the breakdown region. Due to higher temperature and current capability, silicon is preferred in comparison to germanium. The symbol of a zener diode is shown in figure



This is similar to a normal diode except the line representing the cathode is bent at both ends i.e. like the letter z for zener. The V-I characteristics is shown in figure.



When a zener is forward biased its characteristics are just as those of ordinary diode.

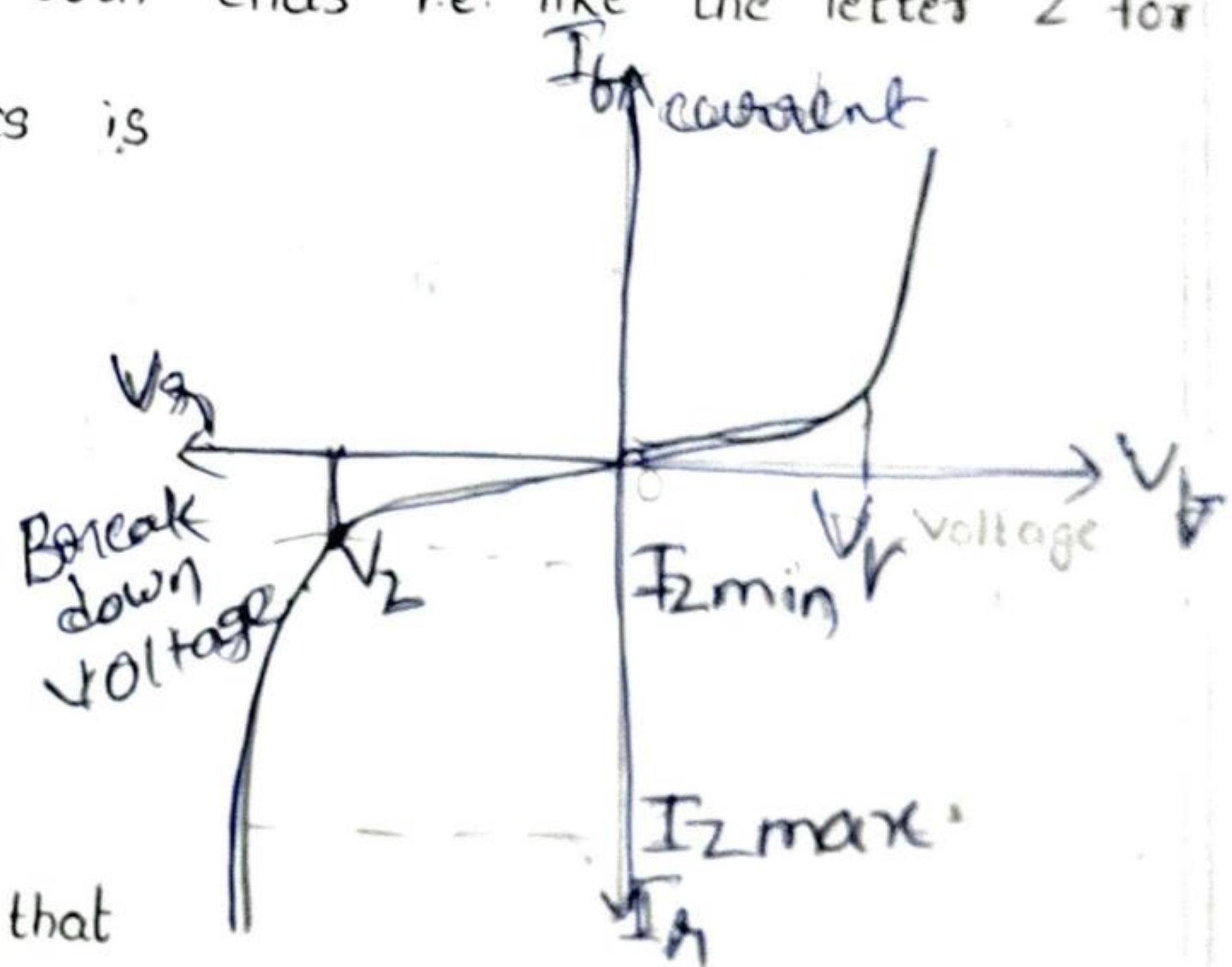It is also obvious from fig. that as the reverse voltage applied to p-n junction is increased, a value is reached at which the current increases greatly from its normal cut-off value. This voltage is called a zener voltage (V_z) or breakdown voltage. So, when a zener diode is reverse biased it has sharp breakdown voltage called zener voltage (V_z).



It is observed from the figure that knee, the breakdown voltage (V_z) remains practically constant. The ability of the diode is called as "regulating ability". The regulating ability of zener diode is an important feature. This feature is used to maintain a constant voltage across its terminal over a operated range of zener current values $I_{z(\min)}$ and $I_{z(\max)}$. We consider the following two important points :-

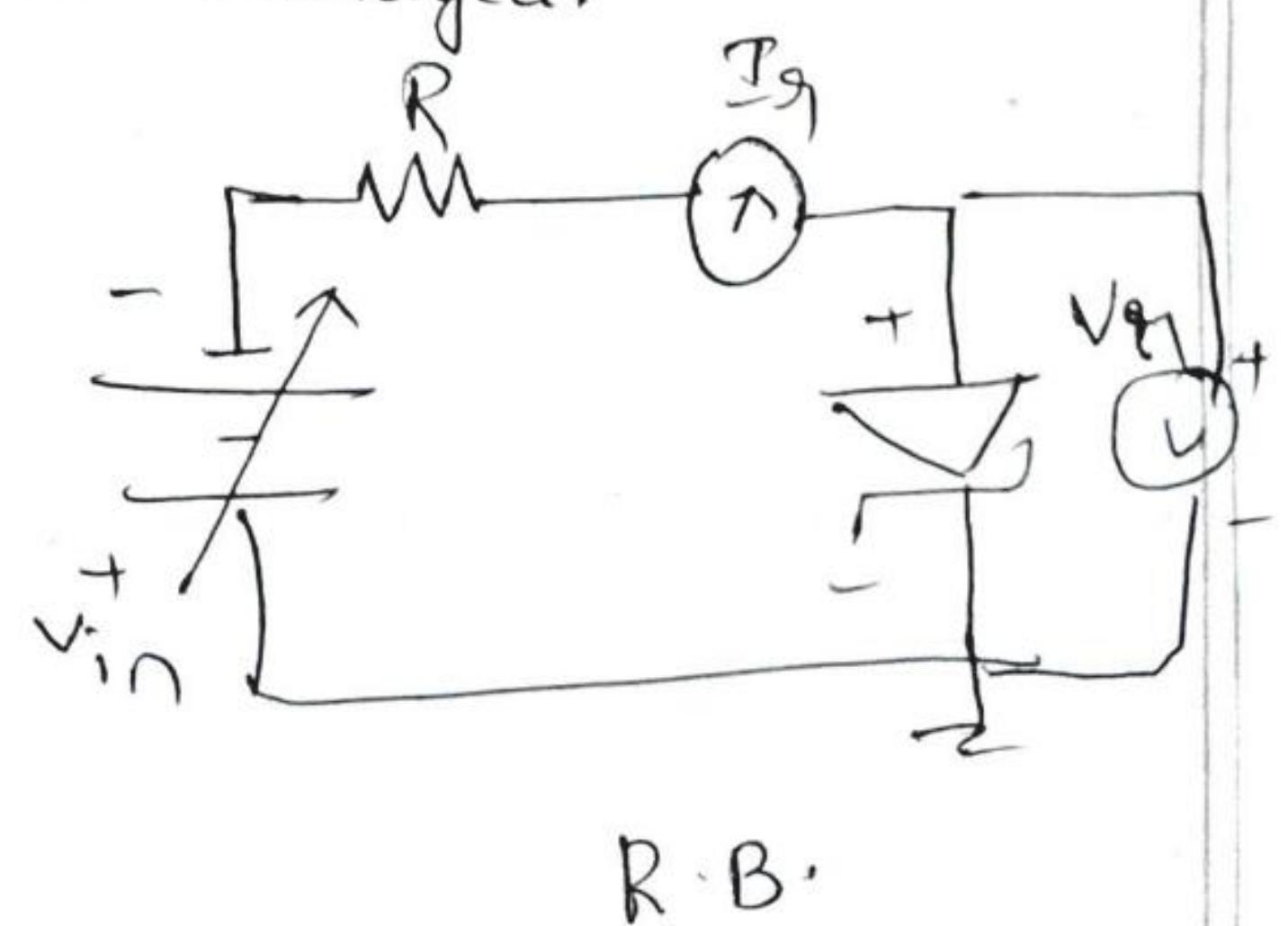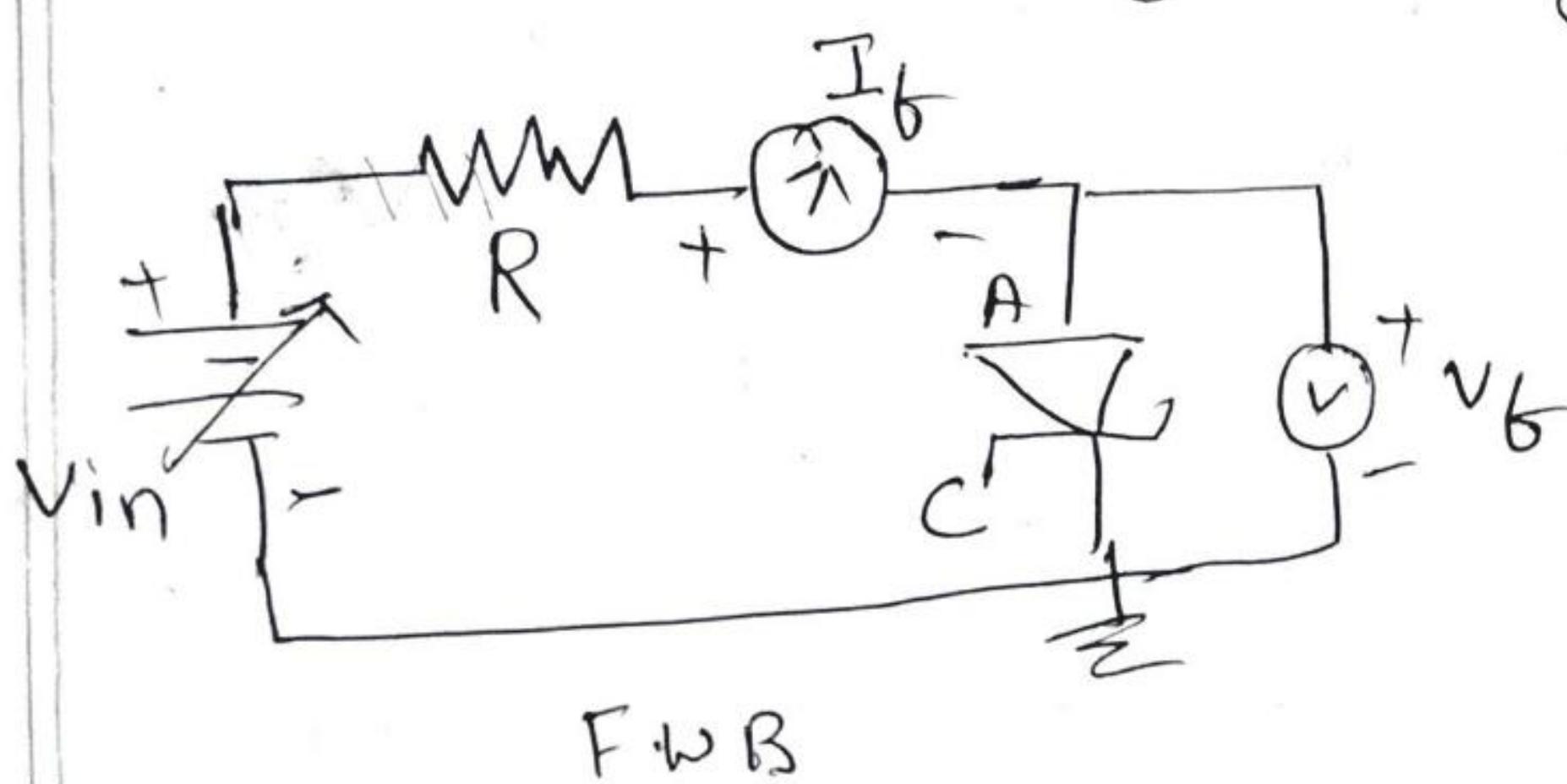- (i) There is a minimum value of zener current $I_{z(\min)}$ called breakover current which must be maintained to keep the diode in breakdown or regulation region. If the current is reduced below the knew of the curve, the voltage changes drastically. So, the regulation is lost.
- (ii) There is a maximum value of zener current $I_{z(\max)}$ above which the zener may be damaged.



②

2

ZENER DIODE SHUNT REGULATOR

↳ A zener diode shunt regulator shown in fig. In the circuit, the series limiting resistance R limits the i/p current.

⇒ The principle of this regulator is that when a zenerdiode operates in breakdown regions (Zener region i.e. $V_{in} > V_z$) The voltage across zenerdiode is constant for a large change in current through it.

⇒ So long as the i/p voltage V_{in} is greater than V_z , the zener operates in breakdown region and maintains constant voltage across R_L even that there is a change in i/p voltage V_{in} or in load current.

Working Of Zener diode shunt Regulator:-

i) Regulation with varying i/p voltage (i.e. R_L fixed).
Let us suppose that i/p voltage $V_{in} \uparrow$ within the limits while the load resistance R_L being fixed.
As V_i increases the i/p current I increases.

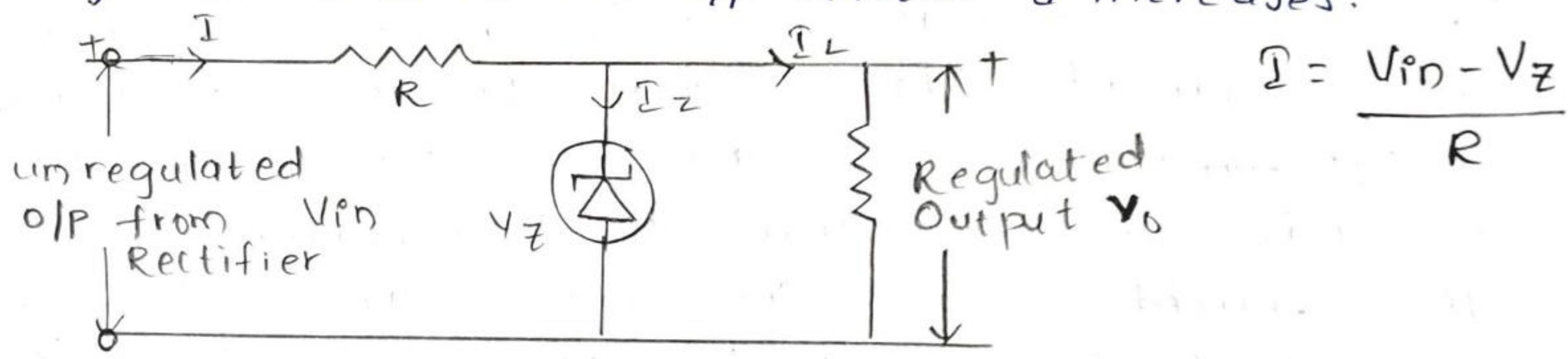


fig: Zener diode shunt Regulator

Now more current flows through zenerdiode i.e. I_z increases of course, load current I_L remains the same. As a result, the voltage drop across R increases in such a way that the voltage across R_L remains constant. On the other hand, if input voltage decreases, the current I also decreases. Now, the current I_z through across R also decreases. Consequently, the voltage drop across R also decreases. As a result, the I_L and

and voltage drop across R_L (V_L) remain constant
 \Rightarrow For fixed value of R_L , the i/p voltage V_i must be sufficiently large to turn the zener diode ON. The minimum turn on voltage $V_{in\ min}$ is determined by,

$$V_z = V_{in\ min} \frac{R_L}{R + R_L}$$

$$V_{in\ min} = V_z \frac{R + R_L}{R_L}$$

V_{max} is limited by zener current $I_{z\ max}$

$$I_R = I_z + I_L \quad \text{or} \quad I = I_z + I_p$$

$$I_{max} = I_{z\ max} + I_L$$

$$V_{in\ max} = V_{R\ max} + V_z$$

$$= I_{max} R + V_z$$

$I_L = \text{fixed}$

$$I_L = \frac{V_z}{R_L}$$

for $R = 0$,

I is max

So,

$$R_{min} = \frac{V_{in\ max} - V_z}{I_{max}} = \frac{V_{in\ min} - V_z}{I_{z\ max} + I_{L\ min}}$$

iii) Regulation with varying load current : [R_L varying]

Let the i/p voltage V_i is kept fixed while the R_L is varies. The variation in R_L produces a change in load current. This in turn produces a change in o/p voltage V_{out} across load. If the load resistance decreases then the load current increases. This current causes the zener current to decrease such that the current I through Resistance "R" is constant.

$$V_{out} = V_{in} - IR$$

This expression shows that o/p voltage being constant since I is constant. On the other hand if the load resistance increases then the load current decreases. This in turn increases the zener current such that the i/p current I and voltage drop R remain constant. Therefore, the o/p voltage remains constant.

③

3

know,

$$V_Z = \frac{V_{in} R_L}{R + R_L} = I_L \cdot R_L = V_o$$

Diode will be in the breakdown voltage region only when $V_{in} \geq V_Z$

When the diode is in the breakdown region $V_o = V_Z$. However, if the load resistance R_L is less than a certain value R_{Lmin} , the voltage $V_o = I_L \cdot R_{Lmin}$ across the R_L may become less than V_Z which implies that diode is not in its operating region.

for example $R_L \rightarrow 0$ (short circuited) $V_o \rightarrow 0$ in order to maintain a constant voltage V_o across R_L for different values of R_L . we have to maintain min value R_{Lmin} of Load resistance to ensure that the zener diode operates in breakdown region.

$$R_{Lmin} = \frac{R V_Z}{V_{in} - V_Z}$$

$$R_{Lmax} = \frac{V_Z}{I_{Lmin}}$$

$$I_{Lmax} = \frac{V_Z}{R_{Lmin}} = \frac{V_{in} - V_Z}{R} \quad R_{Lmin} = \frac{V_Z}{I_{Lmax}}$$

$$I_{Lmin} = I - I_{Zmax} = \left(\frac{V_{in} - V_Z}{R} \right) - I_{Zmax}$$

$$R_{min} = \frac{V_{in max} - V_Z}{I_{Zmax} + I_{L(min)}}$$

$$I_{Zmin} = \frac{(V_{in min} - V_Z)}{R} = I_{Lmax}$$

$$R_{max} = \frac{V_{in min} - V_Z}{I_{Zmin} + I_{Lmax}}$$

R is chosen in such a way that its value should be between R_{max} and R_{min} i.e. $R_{min} < R < R_{max}$

We know,

$$P = V_Z \cdot I_Z$$

The maximum power rating of zener diode :-

$$P_{\max} = V_z I_{z\max} = I_z^2 \cdot R_z$$

(R_z = zenerdiode Resistance)

Zener diode Specifications:-

1. Zener Voltage V_z : The reverse voltage at which reverse current increases sharply is known as zener voltage. Commercially Zener diodes have available ratings from 3V to 200V. The value of breakdown (or zener) voltage depends upon doping. More the doping, lesser the breakdown voltage.
2. Max. Power Dissipation: The max. power dissipation of zener diode is defined as product of zener voltage (V_z) and zener current (I_z) [$P_z = I_z \cdot V_z$]. Every device has a limited capability to dissipate heat energy produced by it. If the power exceeds $P_{z\max}$. The device may burn out.

THYRISTORS

Thyristors are solid state devices which have two or more junctions and which may be switched from ON state to OFF state and vice versa between two conducting states. They are capable of handling large currents upto hundreds of amperes.

The thyristors are divided into the following two types:

1) Unidirectional thyristors :- The thyristors which conduct in forward direction are known as unidirectional thyristors.

Example : Silicon controlled rectifier (SCR)

2) Bidirectional thyristors :- The thyristors which conduct in both directions (forward as well as reverse) are known as bidirectional thyristors.

Example : TRIAC

SILICON CONTROLLED RECTIFIER (SCR)

It is a four layer semiconductor device being alternate of P-type and N-type silicon.


Fig 2(a) shows the structure of SCR while in Fig 2(b) shows symbolic representation

It is obvious from the figure that it consists of three junctions J_1 , J_2 and J_3 (J_1 and J_3 operate in forward direction while middle operates in reverse direction) and three terminals known as anode A, cathode K and gate G.


(Fig : Energy band diagram of two type)

The function of gate is to control the firing of SCR. It conducts only in one direction i.e. from anode to cathode and hence constitutes unidirectional device.

Operation of SCR.

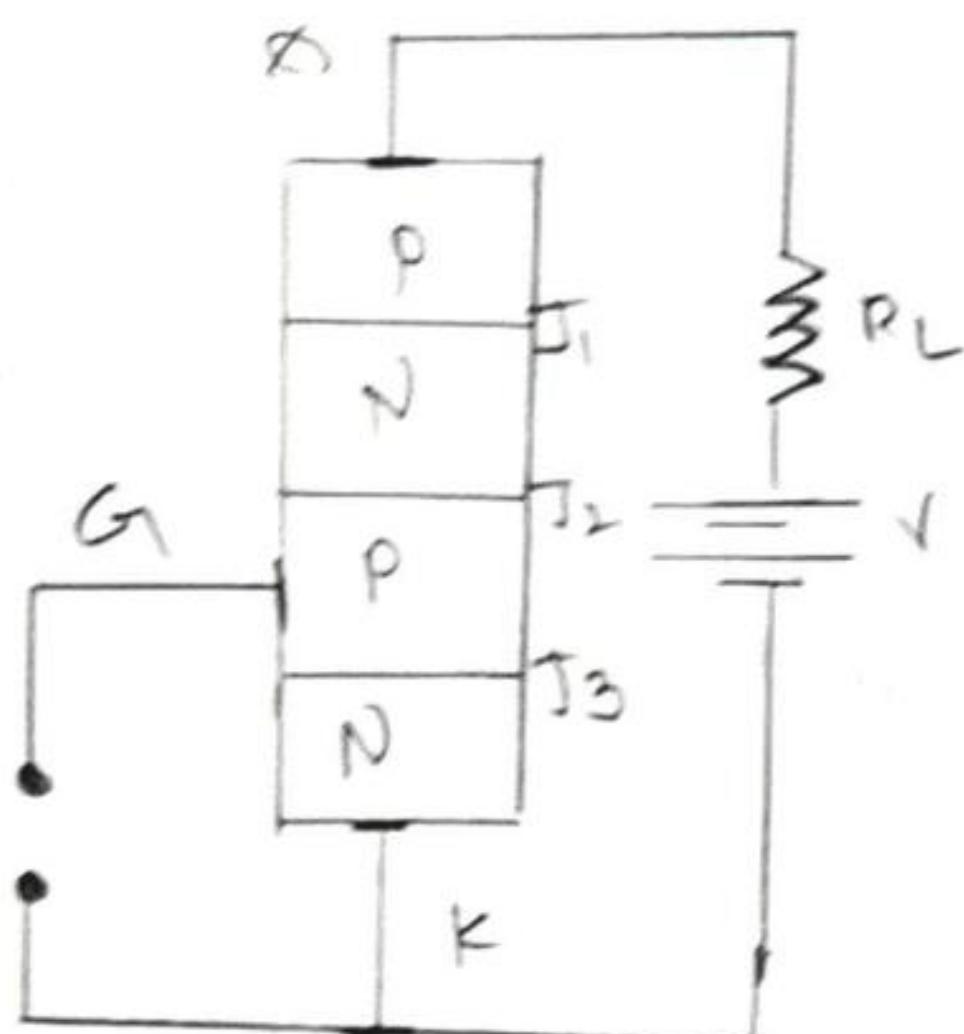

(a) gate is open

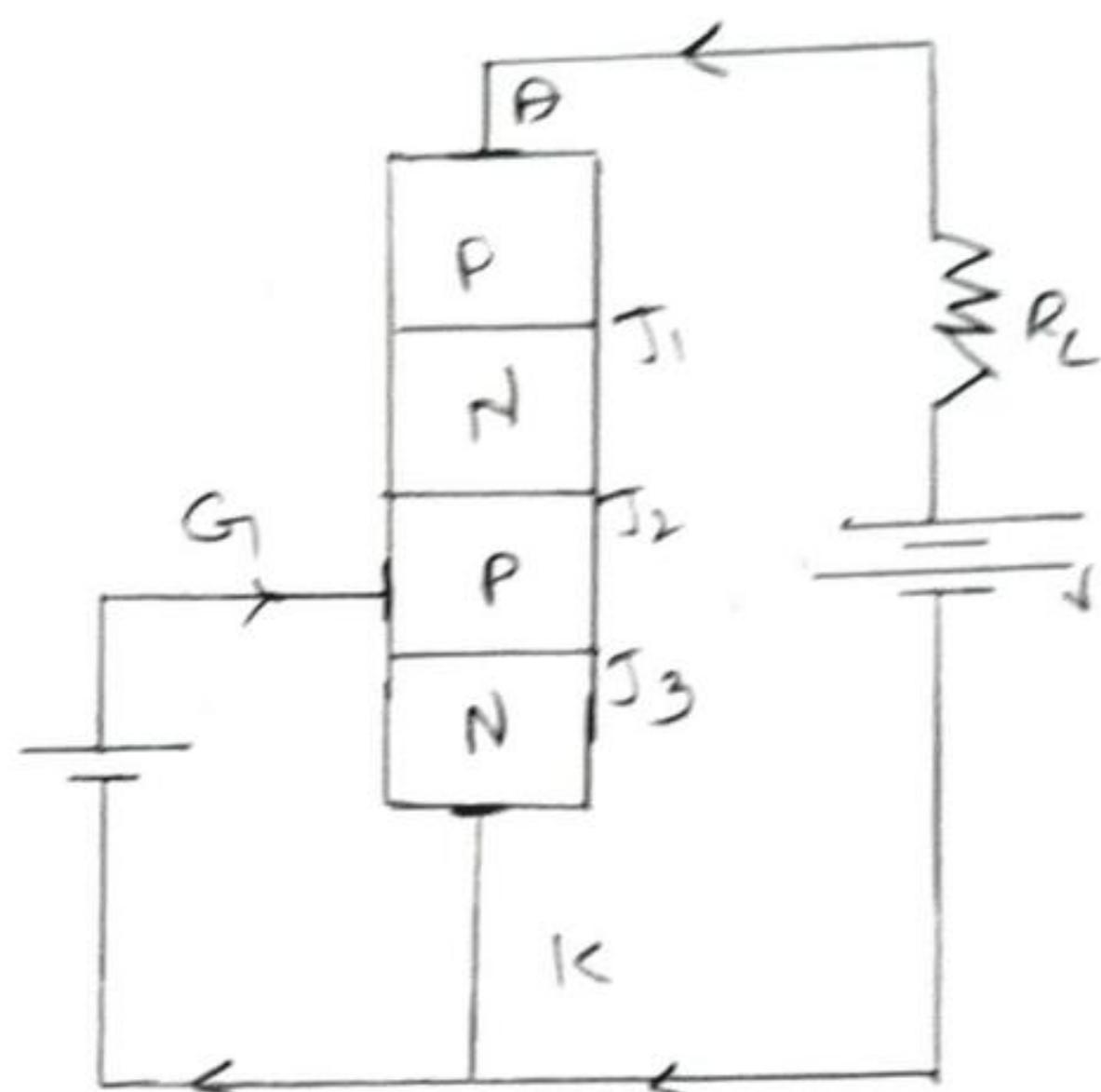


(b) gate is positive

fig (2) operation of SCR

In SCR a load is connected in series with anode and anode is kept at positive potential with respect to cathode with the help of a battery.

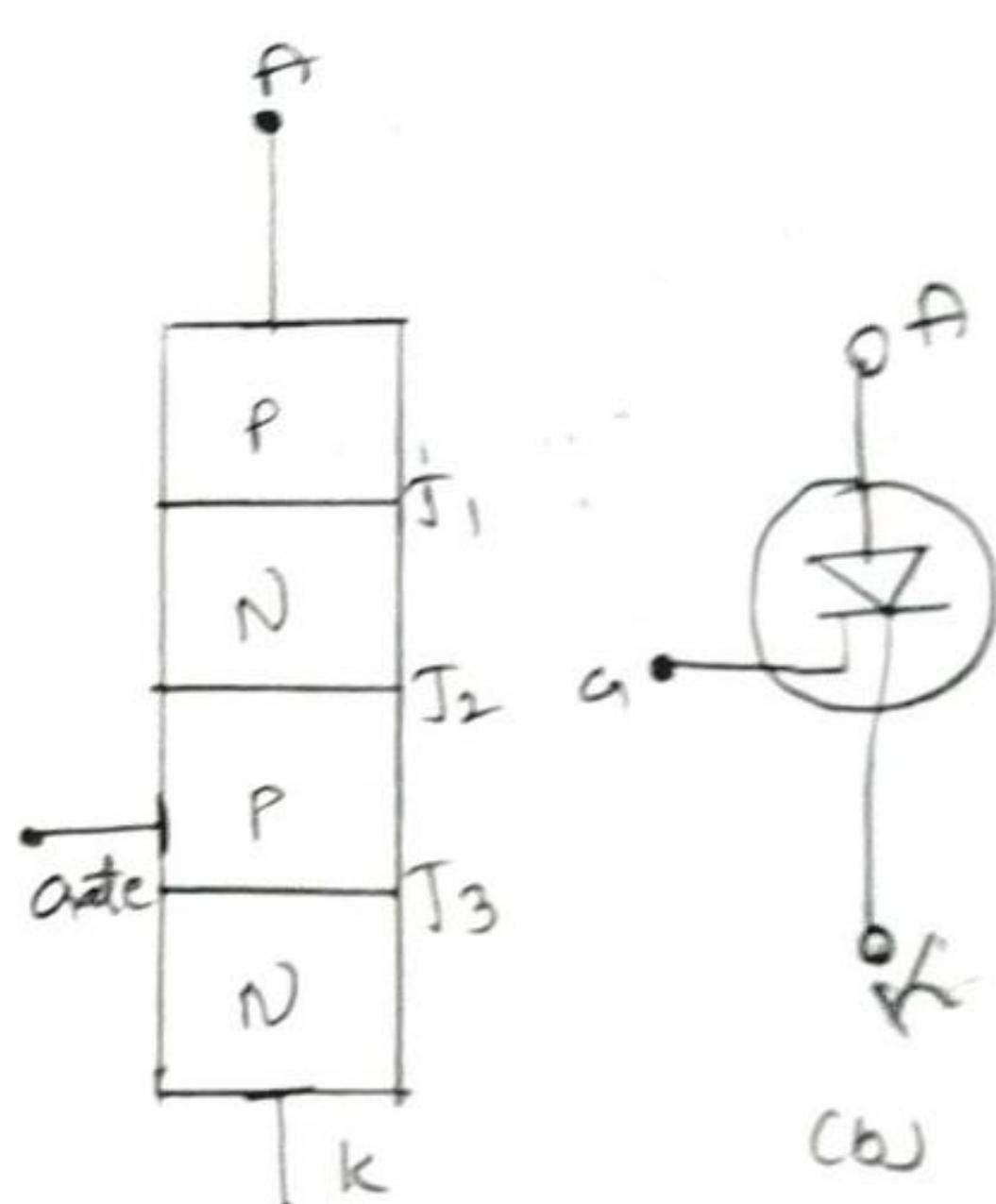The operation of SCR can be studied when the gate is open and when the gate is positive w.r.t cathode. The situations are shown in fig (2).



(a)


Fig (1): structure and symbolic representation of SCR

When the gate is open, no voltage is applied at the gate. Under this condition, junctions J₁

J₃ are forward biased while the junction J₂ is reverse biased. Due to reverse biased of junction J₂ no current flows through R_L and hence the SCR is cut OFF. However when the anode voltage is increased, a certain critical value (Break over voltage) is reached when the junction J₂ breaks down. The SCR now conducts heavily and is said to be ON state. The current is supplied only by the power supply and the load resistance. The current keeps flowing indefinitely.


When the gate is positive w.r.t cathode, junction J₃ is forward biased while junction J₂ is reverse biased. As shown in Fig 2 (b) electrons from n type material move across junction J₃ forward gate while hole from p-type material moves across junction J₃ towards cathode. So gate current, anode current increases. This in turn makes more electrons available at junction J₂. In an extremely small time, junction J₂ breaks down and SCR conducts heavily. Once SCR starts conducting it loses all controls. The current keeps flowing indefinitely until the circuit is open.


VI characteristics of SCR.

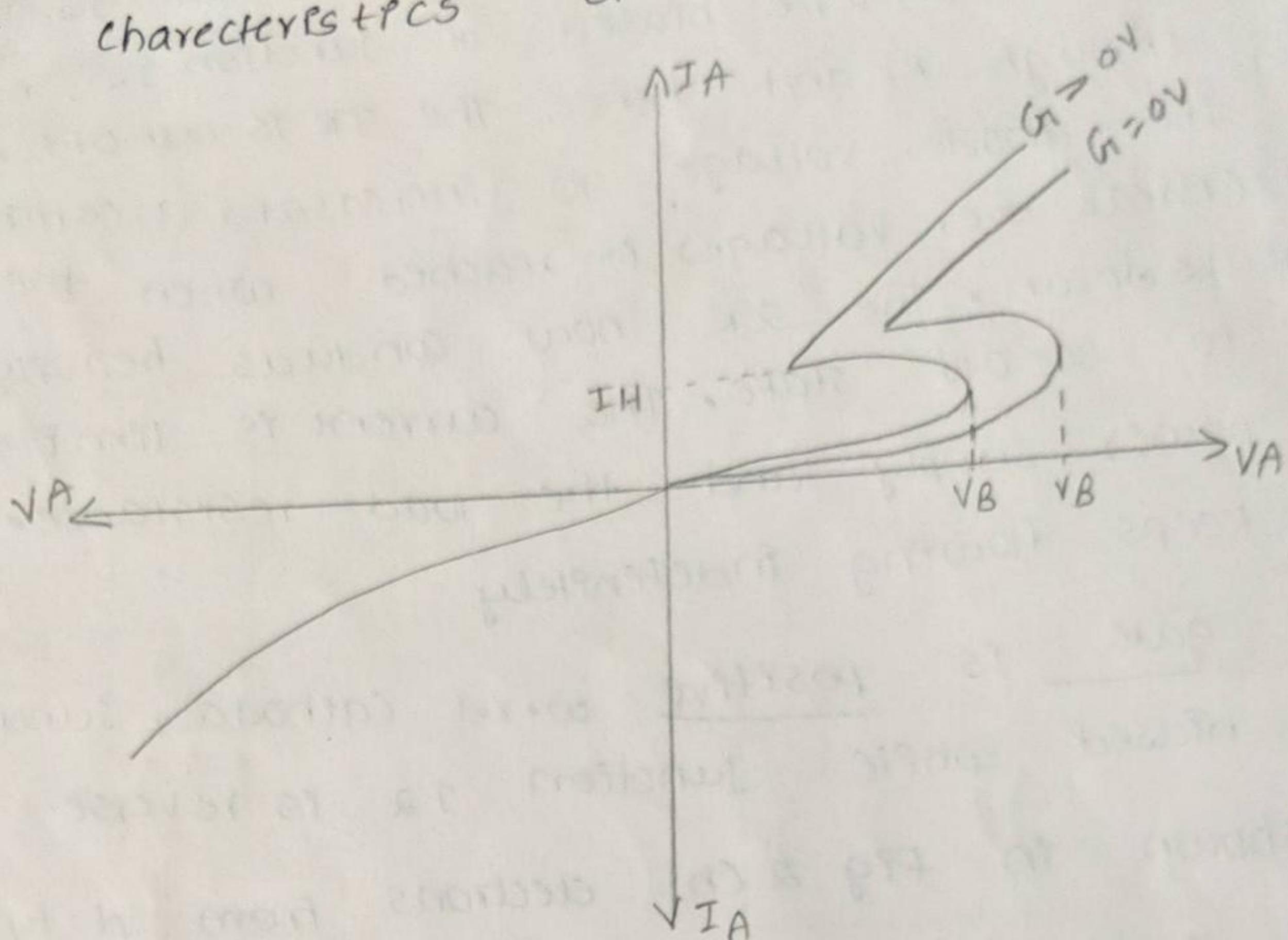

TUNNEL DIODE OR ESAKI DIODE

- A Tunnel diode is a heavily doped diode about 1000 times higher than a normal p-n diode.
- Esaki, a Japanese scientist in 1957 invented such a new diode.
- If doping concentration is increased, its depletion width is decreased by to about 10^{-6} cm and device characteristics are completely changed.
- Under thus condition, many carriers punch through the junction for small amount of forward voltage (i.e less than 0.3V & 0.7V). consequently large forward current is produced. This phenomenon is known as tunnelling.
- This phenomenon utilizes the diode so thin diode is called tunnel diode or Esaki diode.

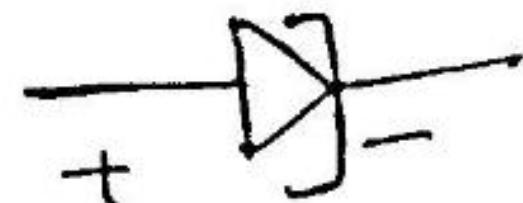
Symbol

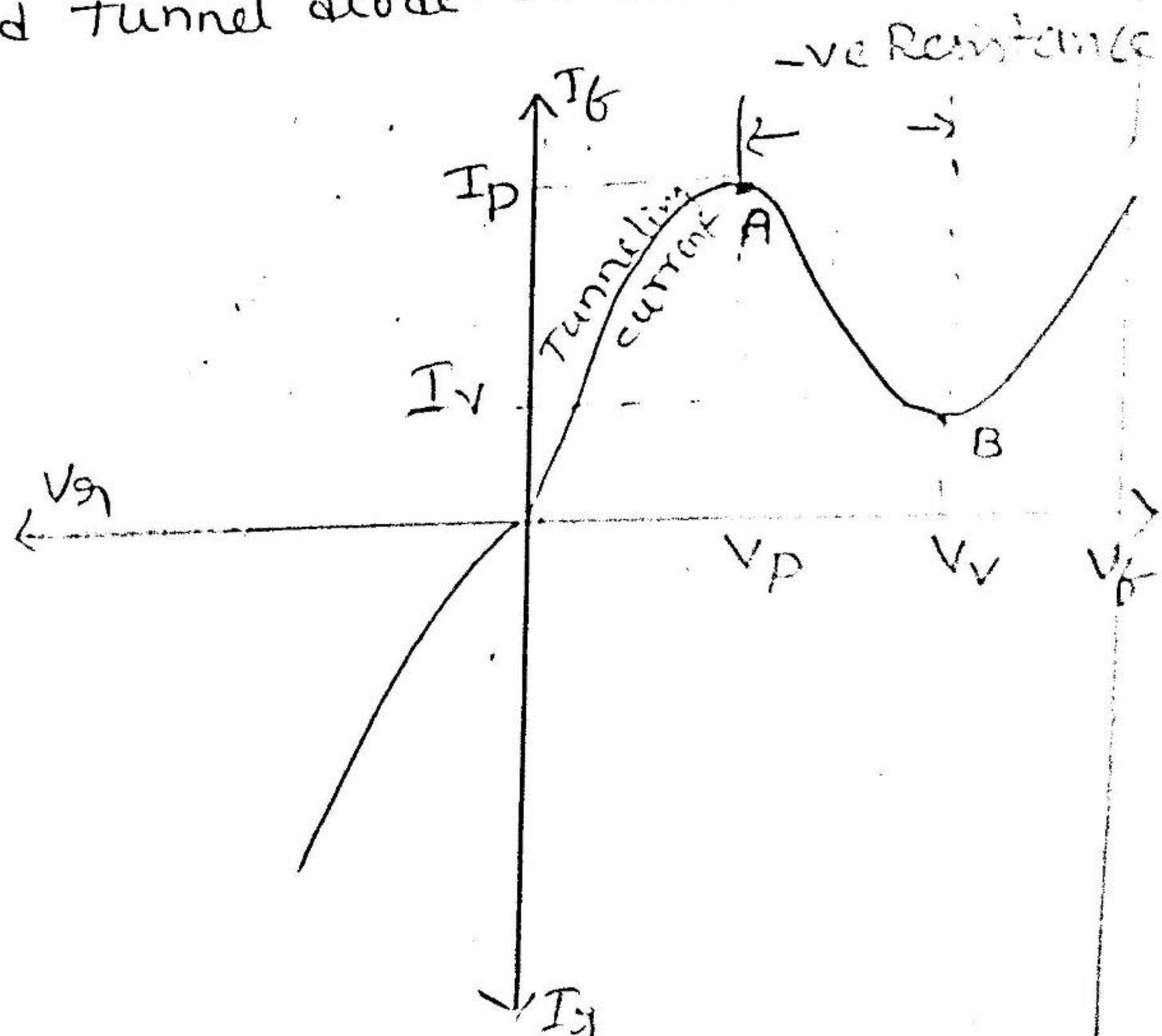

A small forward voltage is applied, large current is produced. The current quickly reaches to its peak value I_p when applied forward voltage reaches to a peak value V_p . It is denoted by point A.

→ When forward voltage is further increased, the diode current starts decreasing. The current decreases to I_v corresponding to valley voltage V_v .

This is denoted by point B.

→ The portion from point A to B, current decreases as voltage increases. So Tunnel diode has -ve Resistance.

→ It is most useful property of the diode because instead of power absorbing, -ve Resistance produces power.



→ Hence Tunnel diode can be used as a very high frequency oscillator.

→ For Greater than V_v , the current starts increasing in case of a conventional diode.

→ If Tunnel diode is reverse biased, it acts as a good conductor i.e. reverse current increases with increase in reverse voltage.

R.B.

FWB

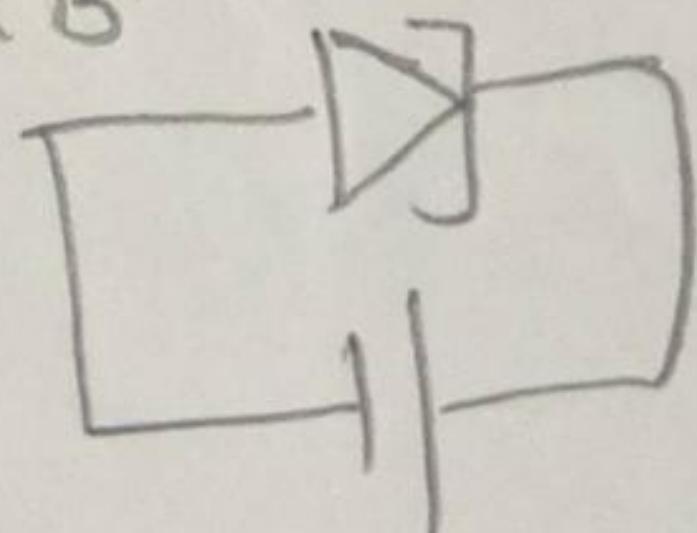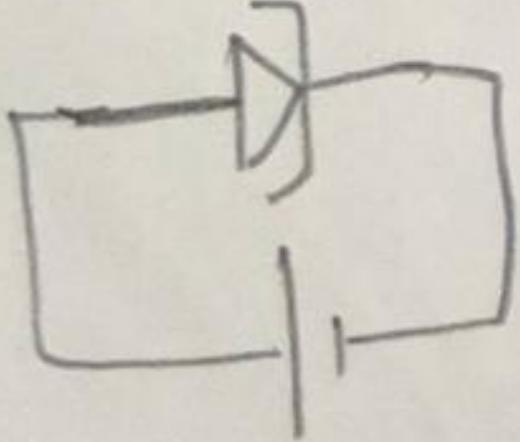

Explanation of V-I characteristics using Energy band diagram

→ Due to heavily doping, In p-type material,

hole concentration is increased in valence band;

In N-Type material e⁻ concentration is increased in conduction band.

→ When P-Type and N-Type materials are joined the energy level diagrams shown in fig. There is a rough alignment of respective valence band and conduction band.

→ No forward current flows across junction when no forward voltage is applied.

→ When a small forward voltage is applied ($\approx 0.1V$), due to upward motion of energy levels of N-region, at the same time downward motion of P-type energy levels. There is some what alignment b/w P & N type energy levels on N-side across the barrier so e⁻ in conduction band of N-side enter in to valence band resulting get some current.

→ Further, Increasing in forward voltage, valence band of P-side and conduction band of N-side there two are in exact alignment. At this stage electrons tunneling through depletion layer with velocity of light and gives rise to large current. This tunneling current reaches to maximum value at a forward bias voltage V_F of the order of $0.1V$.

⇒ After peak voltage V_P , further increase the applied forward voltage, the current starts decreasing because of N-region energy levels are raised so high. again there is out of alignment in b/w two energy levels. Forward voltage reaches to Valley voltage V_V , the tunneling current reaches to minimum values because of out of alignment in b/w P-type energy levels and N-type energy levels.

⇒ B/w Peak current I_P and valley current I_V , Negative

⇒ B/w Peak current I_P and valley current I_V , Negative

② dynamic resistance is obtained.

For voltage greater than V_V , it acts as a

normal P-N junction diode.


Tunneling is much faster than normal crossing. so this is used in ~~faster switch~~ This enables the tunnel diode to switch on and OFF much faster than ordinary P-N diode.

Applications


→ High speed computer memories

→ High frequency oscillators

P-type

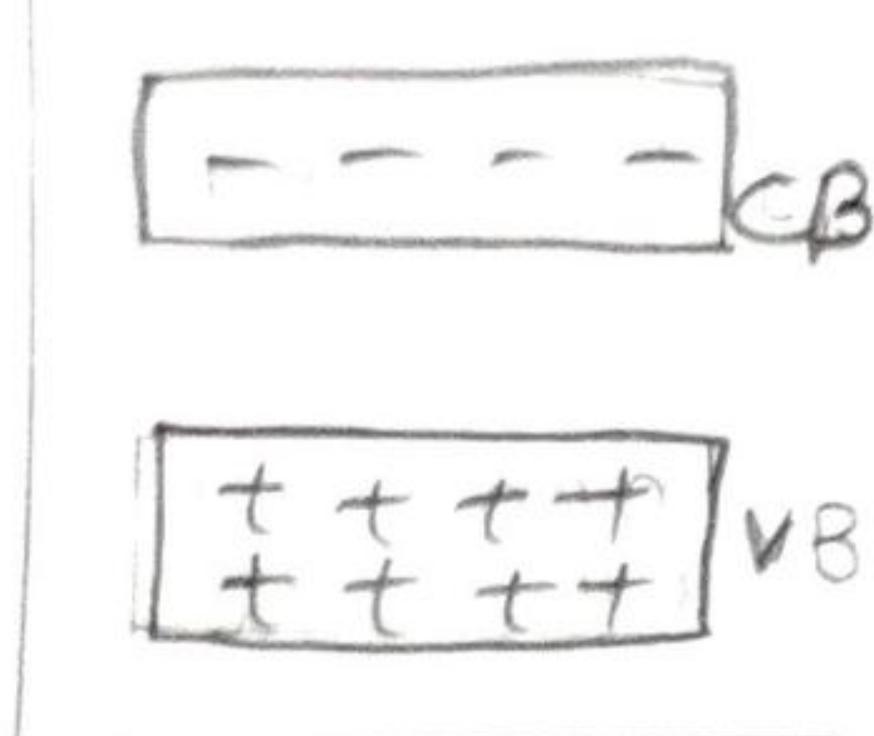


N-type

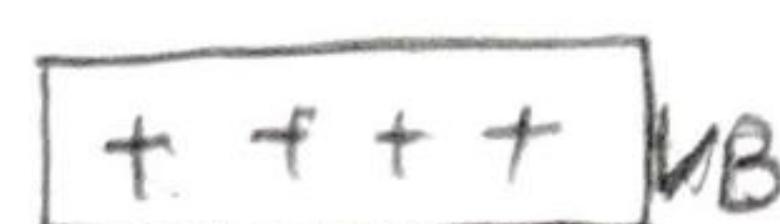


a) Energy band diagram of two types of silicons



b)

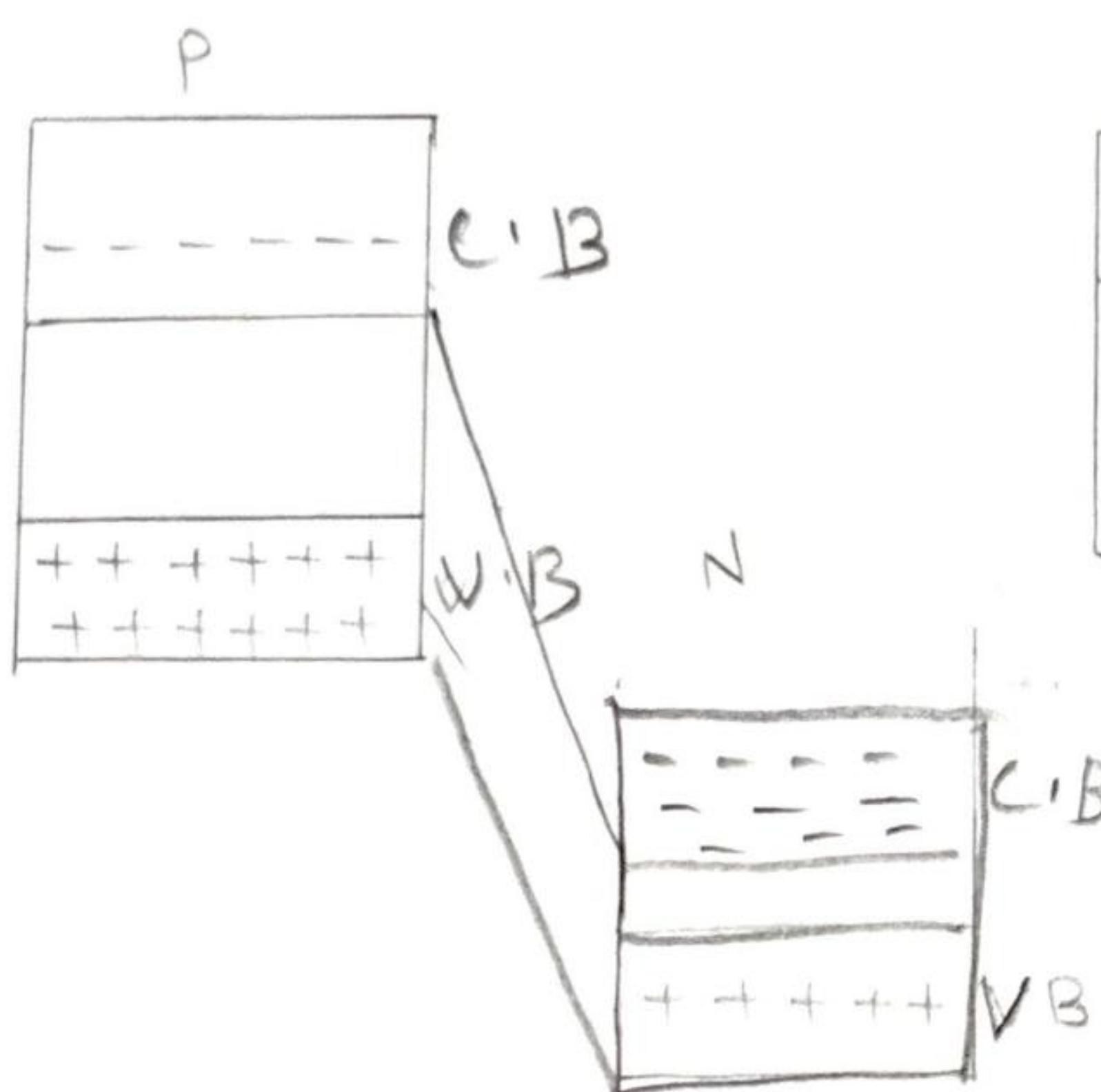

fig(2): Without forward voltage

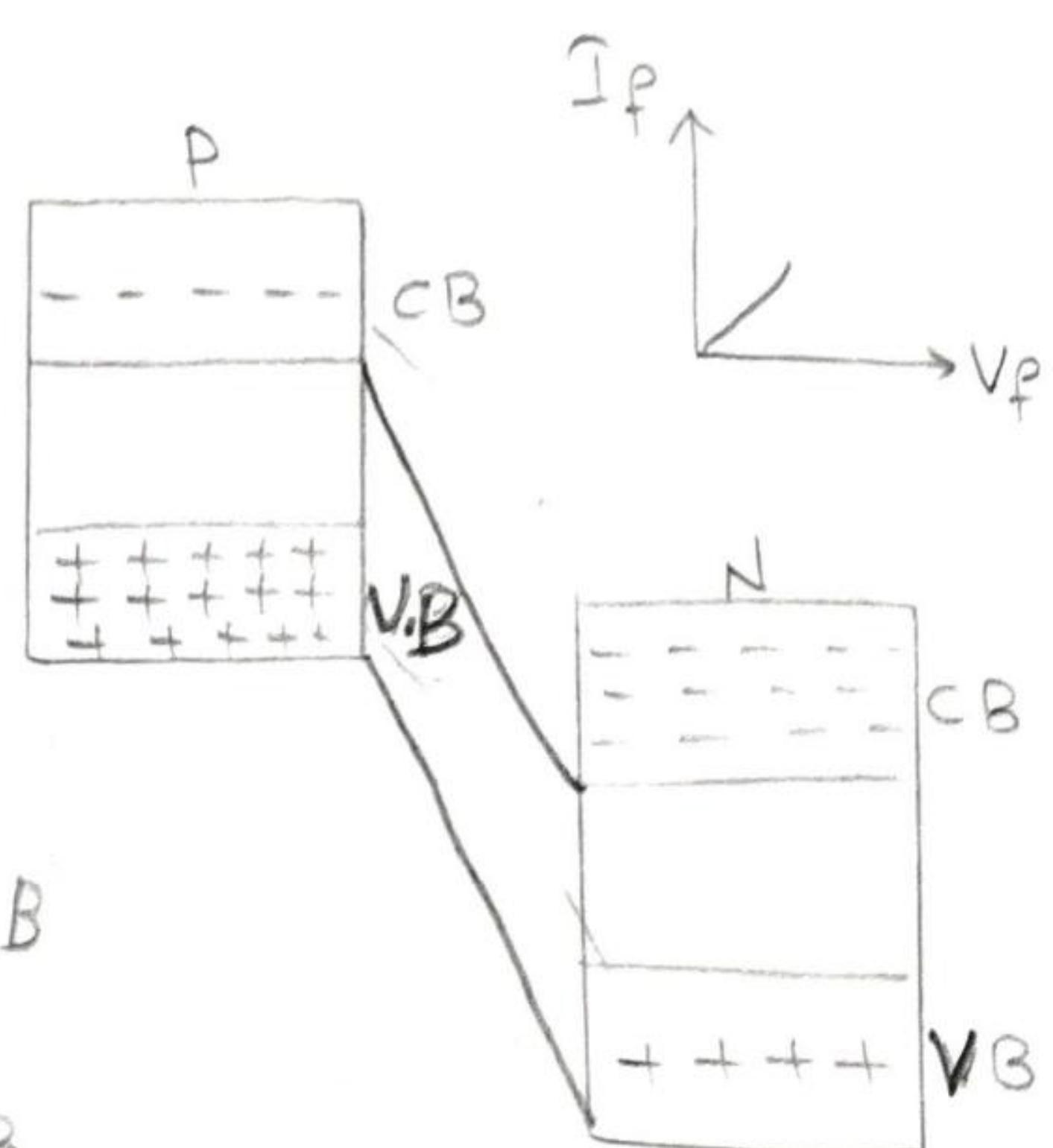

fig(3) small forward voltage

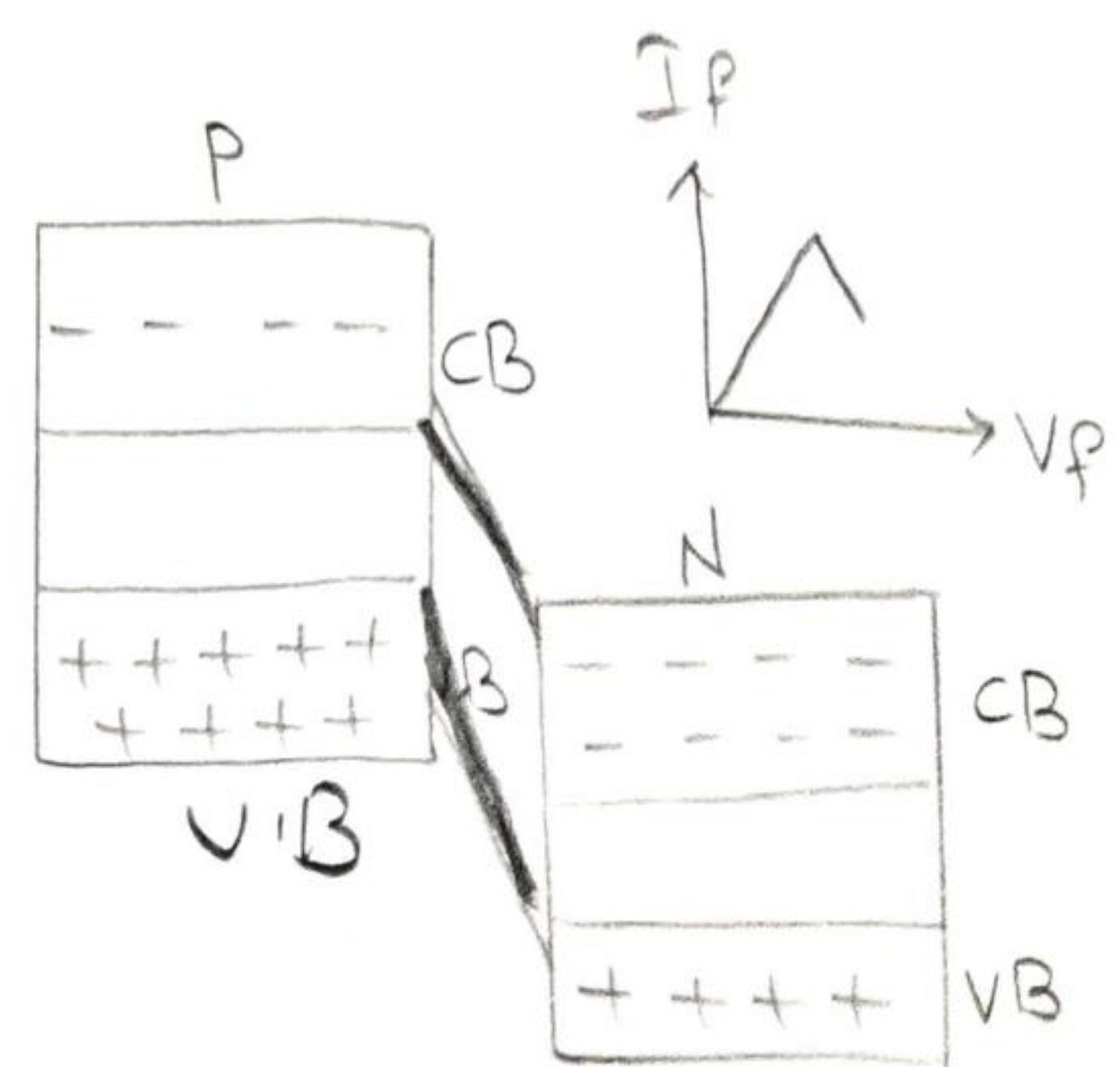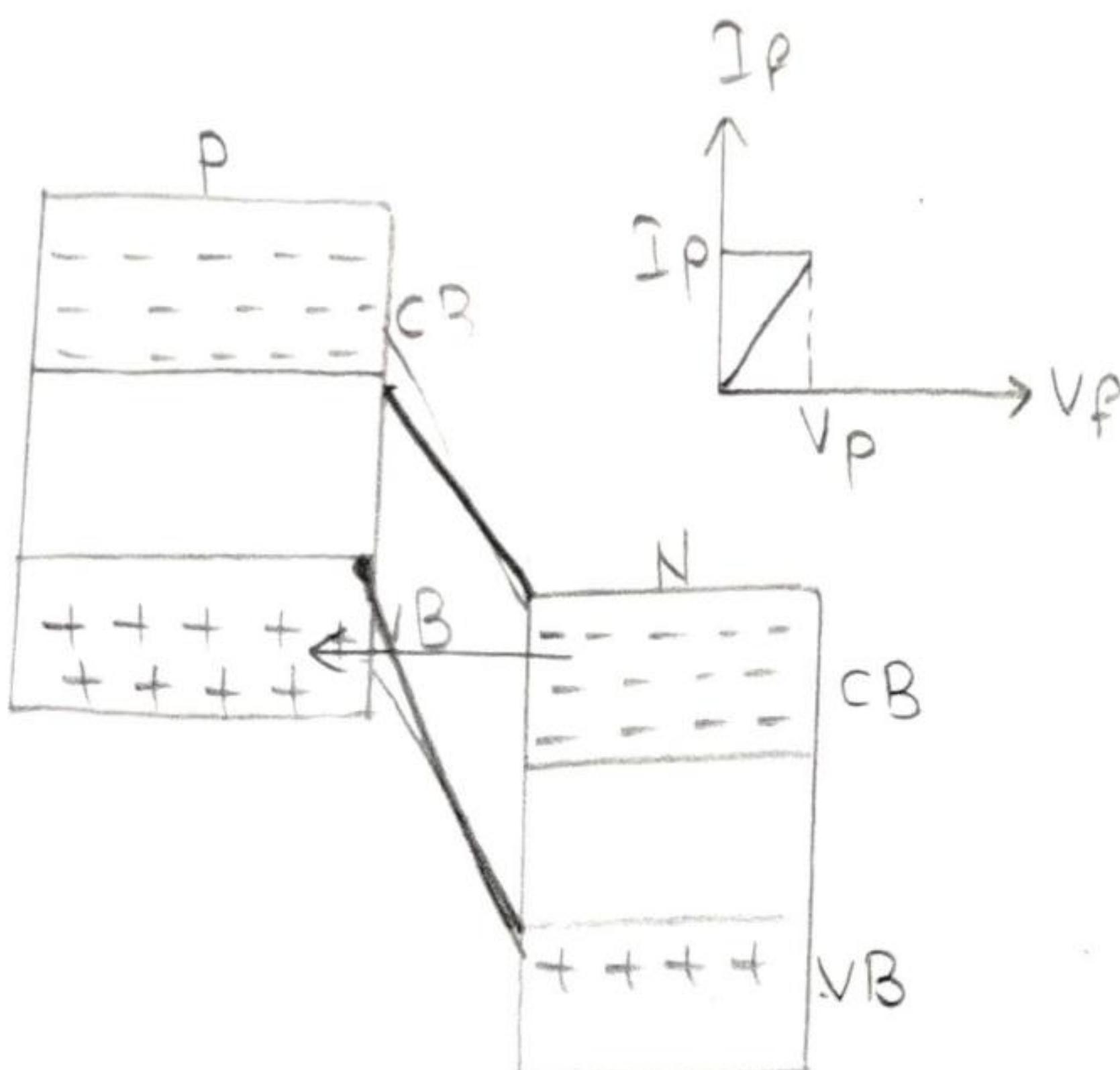

(9)

Varactor diode:

We know that the depletion region in a p-n junction form, biased which separates the positive and negative charges on each side of the junction. Now, the charges can be compared to the charges on the opposite plates of capacitors and the depletion region acting like a dielectric. Thus a p-n junction possesses junction capacitance. When a reverse biased is applied, the junction capacitance decreases because the depletion region width increases. A varactor diode is specially manufactured p-n junction with suitable impurity concentration profile and operated under reverse-biased conditions so as to yield a variable junction capacitance. Special impurity concentration profile ensures negligible junction resistance (which is ordinarily $10\text{ M}\Omega$ or more) in comparison with the capacitive reactance of the junction. These diodes are used in low noise amplifiers, harmonic frequency generators and frequency converters or mixers. The symbol with equivalent circuit is shown in fig (5.27)



(a) symbol




(b) equivalent circuit

Working:

The circuit of reverse biased varactor diode is shown in fig. We know that on applying a reverse bias to junction, the depletion layer created acts as a capacitor dielectric.

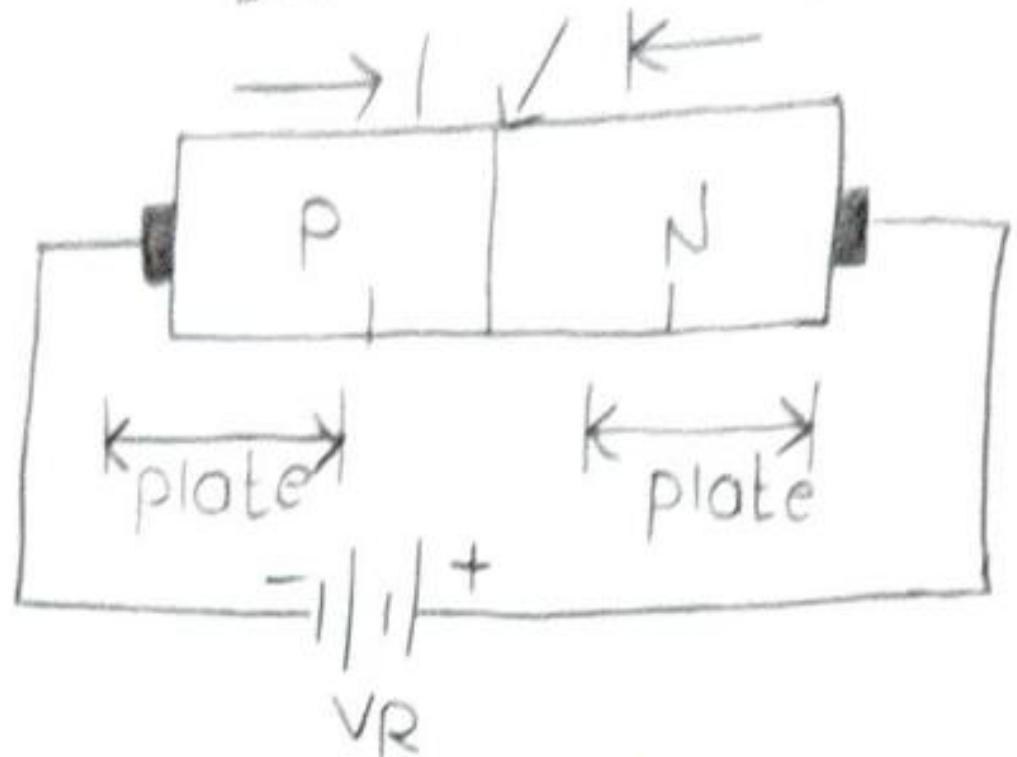and P and N regions as the capacitor plates.
Dielectric (Depletion layer)



When the reverse bias voltage is increased, the depletion layer becomes widened. This increases the dielectric thickness. As a result the capacitance is reduced. On the other hand when reverse bias voltage is decreased, the depletion layer becomes narrower. This decrease the dielectric thickness. In this case, the capacitance is increased.

Figure shows the variation of diode capacitance as a function of applied reverse bias voltage. It is obvious from the figure that the variation of capacitance is maximum when reverse bias voltage is zero and it reduces non-linearly as the reverse-biased voltage increases.

The transition capacitance C_t of a reversed biased p-n junction is given by

$$C_t = \frac{\epsilon A}{\delta x}$$

Where ϵ is the permittivity of the semiconductor material, A is the area of p-n junction and δx is the width of the space charge region. In terms of applied reverse bias V , the transition capacitance is approximated by the following

expression

$$C_T = \frac{k}{(V_T + V)^n}$$

Where, k is the a constant determined by the semiconductor material and fabricated technique, V_T is the volt equivalent temperature, V is the reverse bias applied in Volts. Here $n = (1/2)$ for alloyed junctions and $n = 1/3$ for diffused junctions.

In terms of the capacitance at zero bias condition $C_T(0)$, the capacitance as a function of reverse bias voltage is given by

$$C_T = \frac{C_T(0)}{\left[1 + (V/V_K)\right]^n}$$

Where V_K is the diode barrier potential (e.g 0.7 V for Si)


Types of Varactor diode.

These are two types of Varactor diode profile

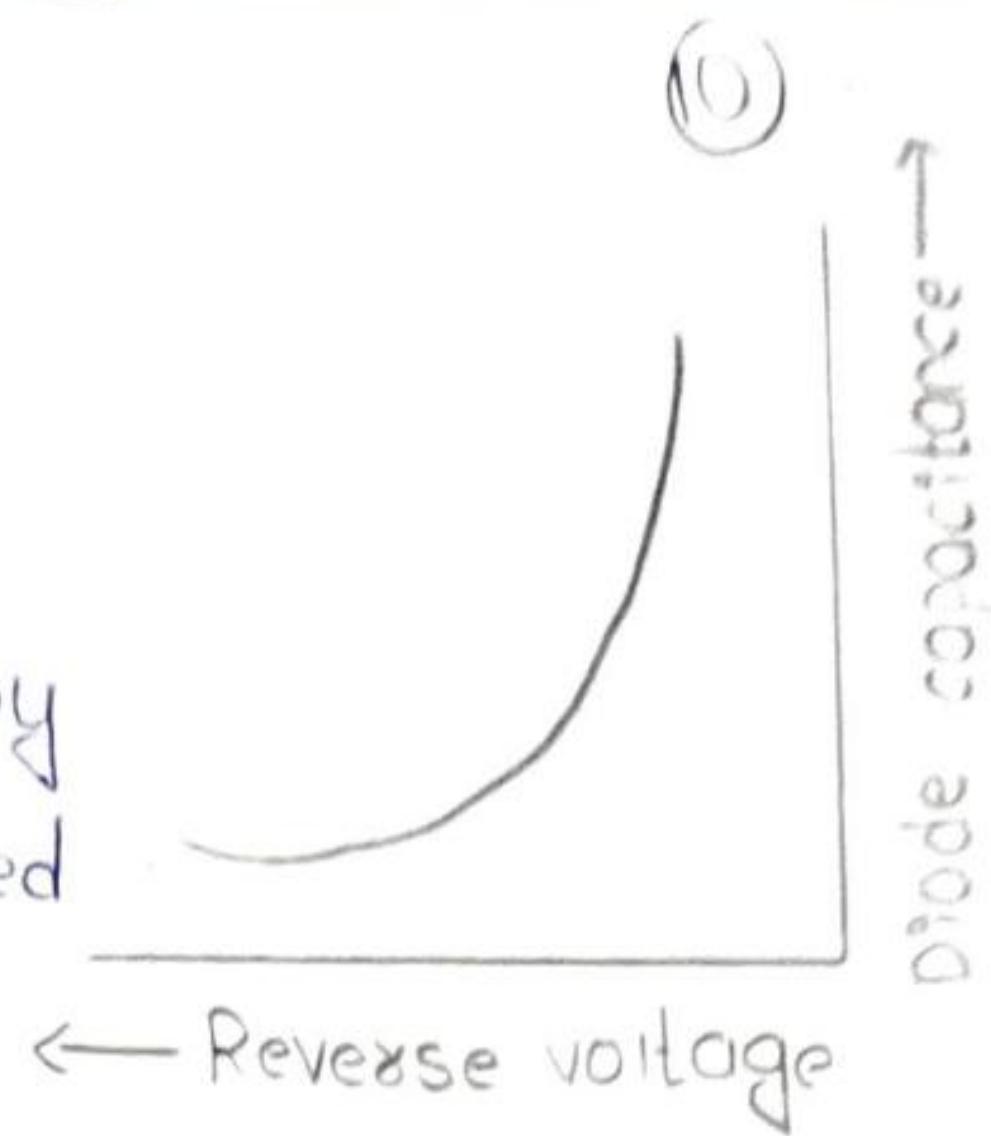i. Abrupt doping profile ii. Hyper abrupt profile.


In abrupt doping profile, the doping is uniform on both sides of junction while in case of hyper abrupt profile, the doping level increases towards the junction as shown in figure.

In case of hyper abrupt profile, due to narrowed depletion layer, a large capacitance occurs at the junction. So, in this case, a small change in reverse bias voltage




makes a larger variation capacitance. Due to this reason, the tuning range for hyper abrupt junction is 10:1. This range is enough to tune a broad cast type receiver over the medium wave band of 550kHz to 1650kHz. It should be remembered that the tuning range of capacitance of an abrupt profile diode is

only uniform doping

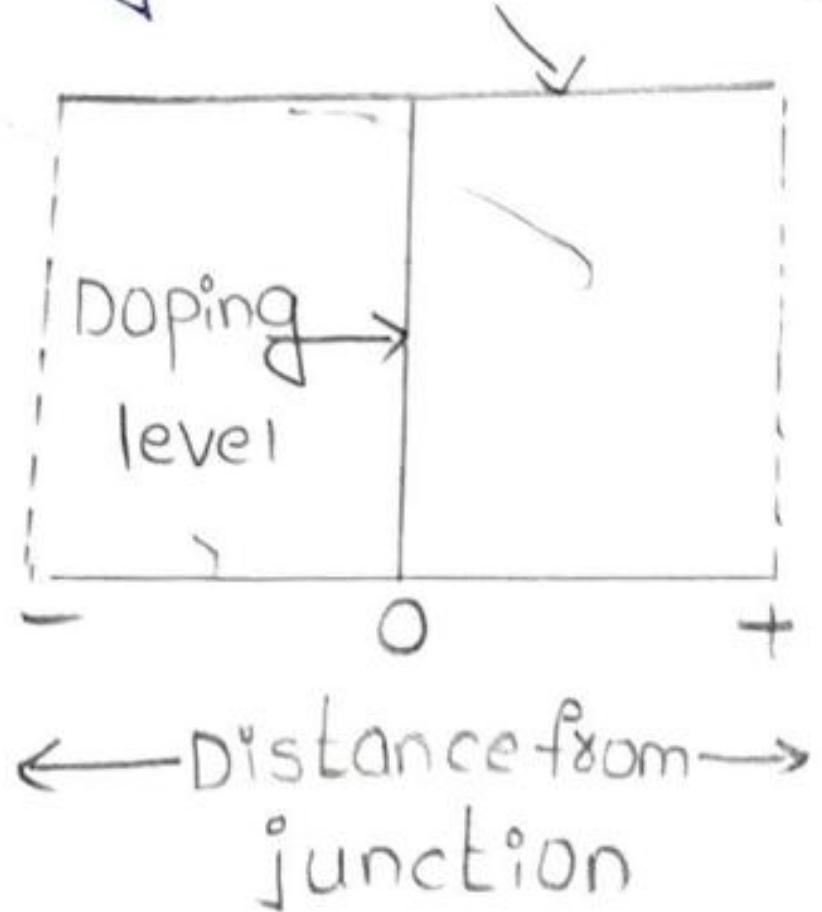

a) Abrupt doping profile

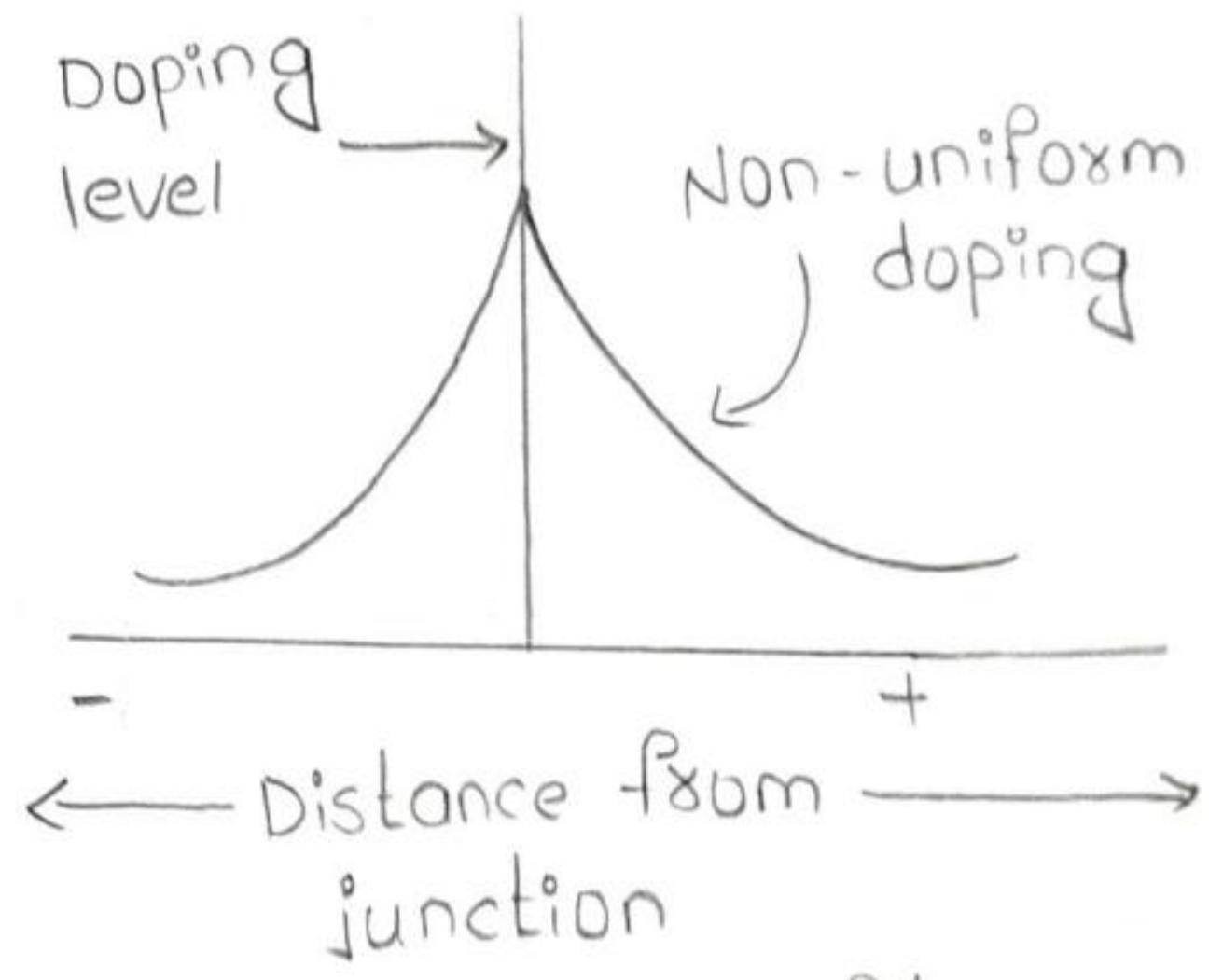

b) Hyper abrupt profile

Applications:

1. used in parametric amplifiers
2. Varactor diode is used in automatic frequency control
3. It is used in tuning circuits
4. used in adjustable band pass filters.