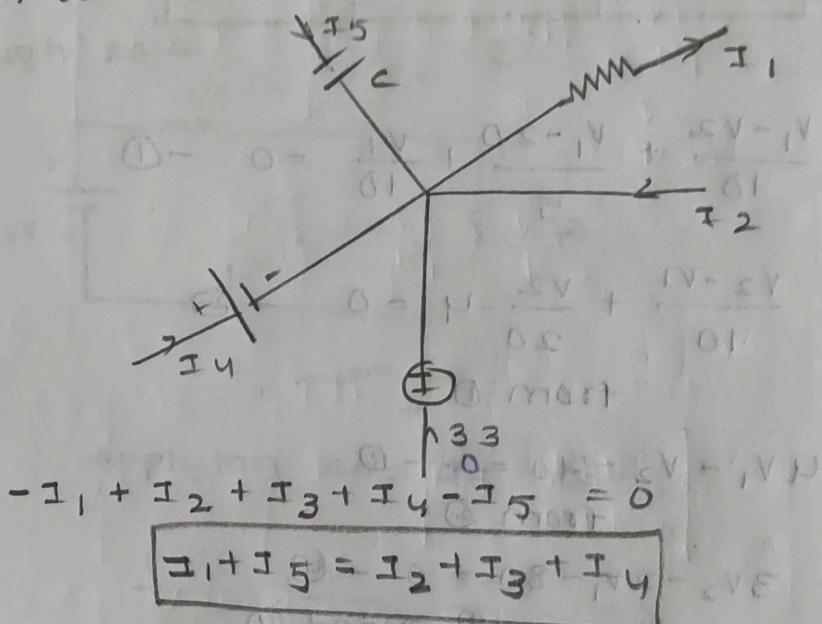



KCL :- This law is also called Kirchhoff's junction rule. It states that the algebraic sum of the current meeting at a junction node is equal to zero

(or)

The sum of the current entering at node is equal to the sum of the current leaving that node.



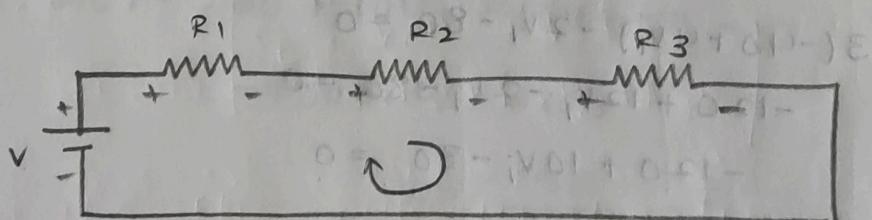KVL :- This law is also called as Kirchhoff's loop rule. It states that the algebraic sum of potential difference around a closed circuit must be zero.



Apply KVL to loop :-

$$-V_1 - V_2 - V_3 + V = 0$$


$$V = V_1 + V_2 + V_3$$

$$V = IR_1 + IR_2 + IR_3$$

$$V = I(R_1 + R_2 + R_3)$$


$$I = \frac{V}{R_1 + R_2 + R_3}$$

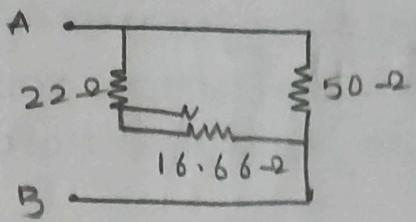b) calculate the effective resistance b/w the terminals A and B?



Let
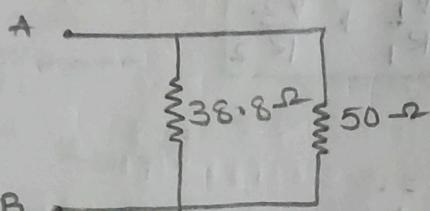
$$\begin{aligned} R_A &= R_1 + R_2 \\ &= 22 + 16.6 \\ &= 38.8 \Omega \end{aligned}$$




Let

$$\begin{aligned} R_{AB} &= \frac{R_1 \times R_2}{R_1 + R_2} \\ &= \frac{38.8 \times 50}{38.8 + 50} = \frac{1930}{88.6} = 21.8 \Omega \end{aligned}$$

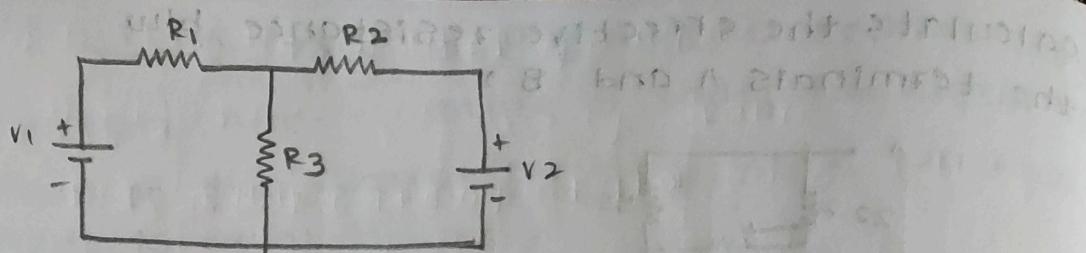
2) State and explain Norton's theorem,

Any two terminal linear bilateral network can be replaced by an equivalent circuit consist of an equivalent source in parallel with resistance  $R_n$ .

where  
 $I_{sc}$  is a short circuited current measured through the load terminal  $R_n$  is the Norton's equivalent resistance measured across the load terminal when all the sources are replaced by their internal resistance.



To find  $I_{N1}$ :

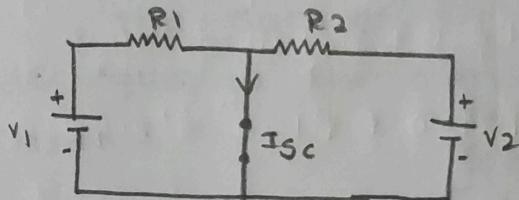


$$I_{SC} = I_1 + I_2$$

$$I_1 = \frac{V_1}{R_1}$$

$$I_2 = \frac{V_2}{R_2}$$


$$I_{SC} = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

To find  $R_N1$ :

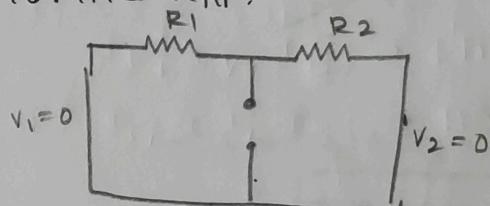

$$R_N1 = \frac{R_1 R_2}{R_1 + R_2}$$

Morton's equivalent:

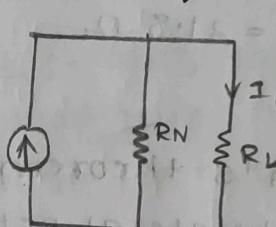


$$I_L = \left( \frac{V_1 R_2 + V_2 R_1}{R_1 R_2} \right) \times \left( \frac{R_1 R_2}{R_1 + R_2} \right)$$



$$I_L = \frac{V_1 R_2 + V_2 R_1}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

State the superposition principle?

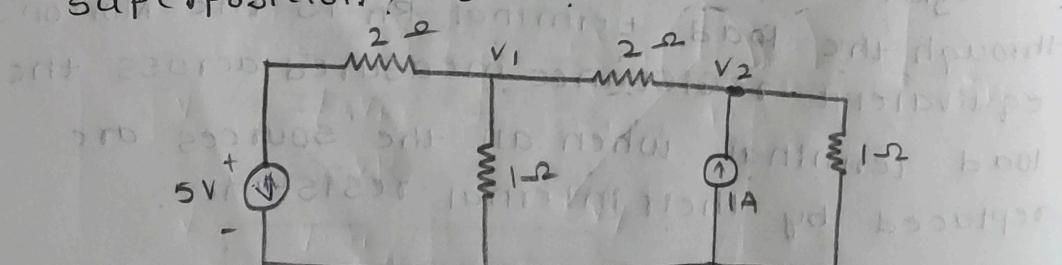Determine the current in all resistors using superposition theorem?



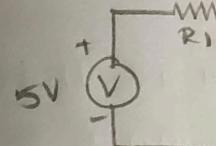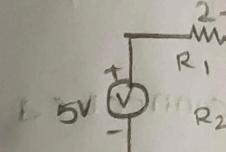
It states  
containin  
in any e  
of respon  
acting at  
zero.  
case i:-



$$I_{1-i} = 1$$

$$I_{2-i} = I_1$$

case iii

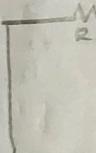

Ra



Rb

$$I_1'' =$$

$$I_2''$$

It states that in any linear network containing two or more sources, the responses in any element is equal to the algebraic sum of responses caused by individual sources acting alone, while the other source are kept zero.

case i :- Remove IA

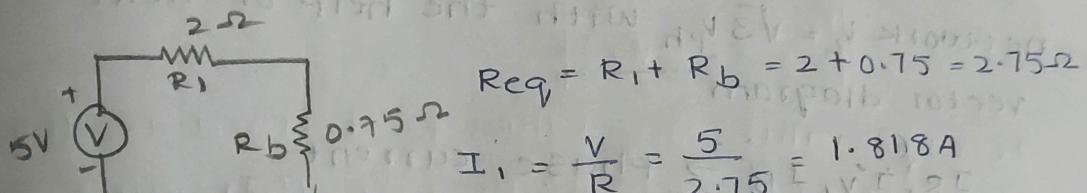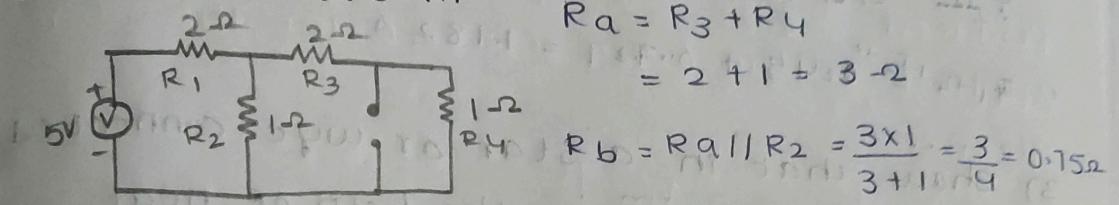


$$I_T = 1.82 A$$


$$I_{1''} = 1.82 \times \frac{3}{3+1} = 1.365 A$$

$$I_{2''} = I_1' = 1.82 - 1.365 = 0.455 A$$

case iii:-

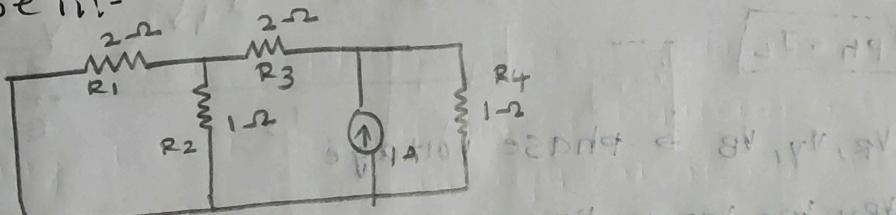
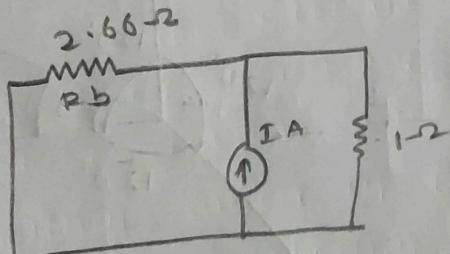
$$R_b = Ra + R_3 = 0.66 + 2 = 2.66 \Omega$$



$$I_1''' = I_1 \times \frac{R_b}{R_b + 1} = 1 \times \frac{2.66}{2.66 + 1} = 0.726 A$$

$$I_{2'''} = 1 - 0.726 = 0.271 A$$

$$I_2'' = 0.272 - 0.181j = 0.09A$$

case 3:- the sum of three components

$$I_{2-2} = 1.82 + 0.09 = 1.91A$$

$$I_{1-2} = 1.365 + 0.1818 = 1.546A$$

$$I_{2-2} = 0.455 + 0.272 = 0.727A$$

$$I_{1-2} + I_{2-2} = 0.45 + 0.727 = 1.182A$$

3) Show that in a star or wye connected network  $V_L = \sqrt{3} V_{ph}$  with the help of neat vector diagram.

$I_R, I_Y, I_B \rightarrow$  phase current


$I_1, I_2, I_3 \rightarrow$  line currents

$$I_R = I_1$$

$$I_Y = I_2$$

$$I_B = I_3$$

$$\boxed{I_{ph} = I_L}$$

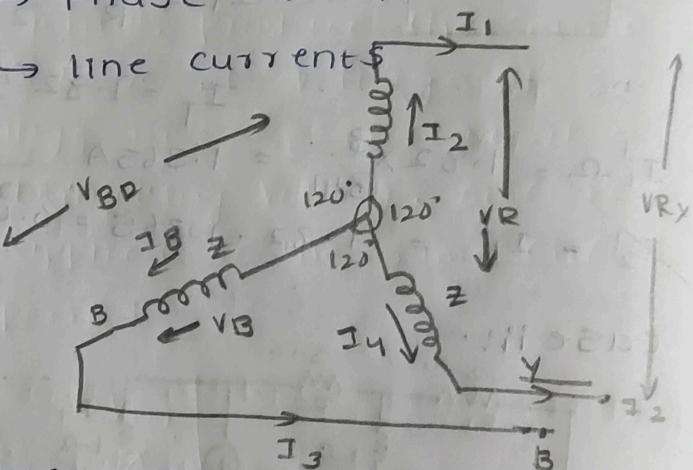

$V_R, V_Y, V_B \rightarrow$  phase voltage

$V_{RY}, V_{RB}, V_{BR} \rightarrow$  line voltage ( $V_L$ )

$$V_{RY} = V_R - V_Y$$


$$\frac{1}{2}(V_L)$$

$$\cos 30^\circ = \frac{OC}{OA}$$

$$\frac{\sqrt{3}}{2} = \frac{\frac{1}{2}V_{RY}}{VR}$$

$$\frac{\sqrt{3}}{2} = \frac{\frac{1}{2}V_L}{V_{ph}}$$
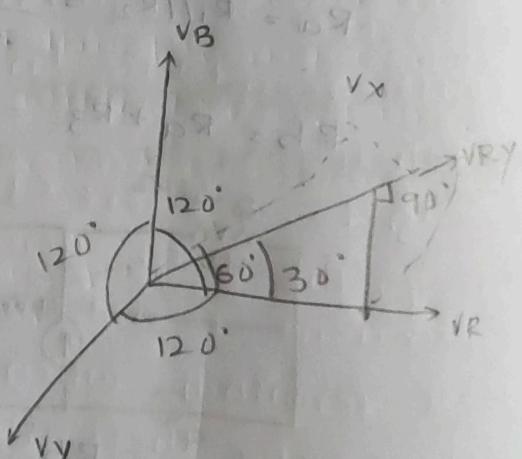
$$\sqrt{3} = \frac{V_L}{V_{ph}} \quad \boxed{V_L = \sqrt{3}V_{ph}}$$



4) Define power factor? What is its significance?  
It is the ratio of watts that are to the volt amperes that are fed into the circuit.

Power factor =  $\frac{\text{Active power}}{\text{Apparent power}}$

$$P.f = \frac{P}{S} = \frac{V \cdot I \cos \phi}{V \cdot I} = \cos \phi$$

$$P.f = \cos \phi$$

b) Distinguish b/w ideal and practical transformer? A single phase 250KVA 50Hz transformer having the voltage ratio of 1100V/415V. Then calculate primary and secondary current.

Transformer KVA = 250KVA  
frequency = 50Hz

$$\frac{V_1}{V_2} = \frac{1100}{415}$$

Primary current  $I_1 = \frac{KVA}{V_1}$

$$= \frac{250}{1100} = 0.22$$

Secondary current  $I_2 = \frac{KVA}{V_2}$

$$\frac{250}{415}$$

$$= 0.602,$$

5) Define the following

i) RMS value ii) Average value


RMS value - RMS value of an AC voltage is defined as that constant voltage, which produces the same amount of heat energy as produced by AC voltage, when both are applied to the same circuit for the same period.

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

Average value - Avg value is defined as that constant value, which produce the same amount flux increase of voltage or same amount of change in case of current as produced by alternating voltage or current when both are applied to the same circuit for the same period.

$$V_{\text{avg}} = \frac{2V_m}{\pi}$$

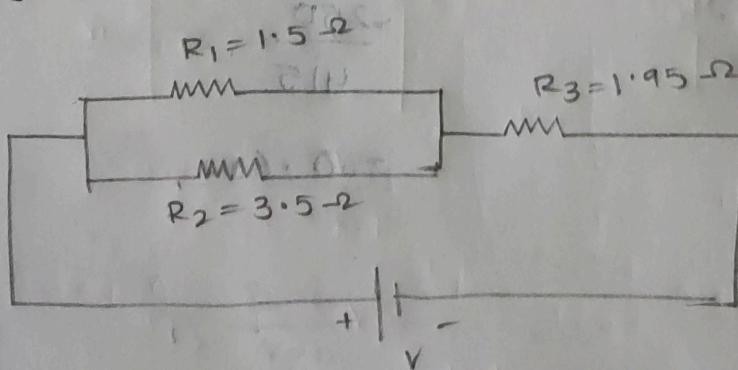5b) Two resistances of  $1.5\Omega$  and  $3.5\Omega$  are connected in parallel and this parallel combination is connected in series with a resistance of  $1.95\Omega$  calculate the equivalent resistance value




$$R_a = \frac{V}{I} = \frac{R_1 + R_2}{R_1 + R_2 + R_3} = \frac{1.5 + 3.5}{1.5 + 3.5 + 1.95} = \frac{5.25}{5.25 + 1.95} = 1.05 \Omega$$

$$R_{eq} = R_a + R_3 = 1.05 + 1.95 = 3 \Omega$$

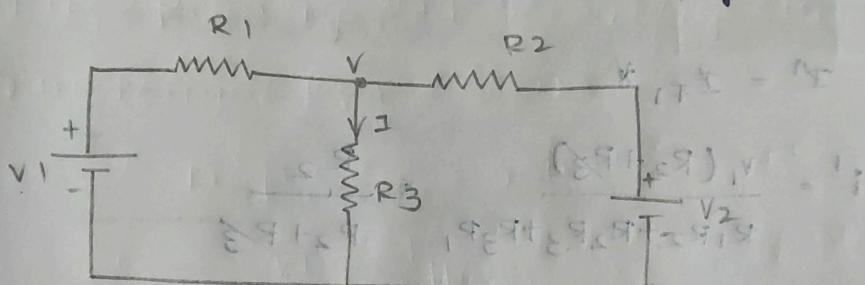b) State and explain superposition theorem,  
 It states that in any linear network containing two or more sources, the response of any element is equal to the algebraic sum of responses caused by individual source acting also while the other sources are kept at zero verification:-

Let us find the current flowing through resistance  $R_3$ . Let the node voltage be.



Applying KCL to fig

$$\frac{V - V_1}{R_1} + \frac{V}{R_3} + \frac{V - V_2}{R_2} = 0$$

$$V = IR_3$$


$$\therefore \frac{IR_3 - V_1}{R_1} + \frac{IR_3}{R_3} + \frac{IR_3 - V_2}{R_2} = 0$$

$$I \left[ \frac{R_3}{R_1} + \frac{R_3}{R_2} + 1 \right] = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

~~Let us consider  $V_1$  acting alone~~

$$I \left[ \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1 R_2} \right] = \frac{V_1 R_2 + V_2 R_1}{R_1 R_2}$$
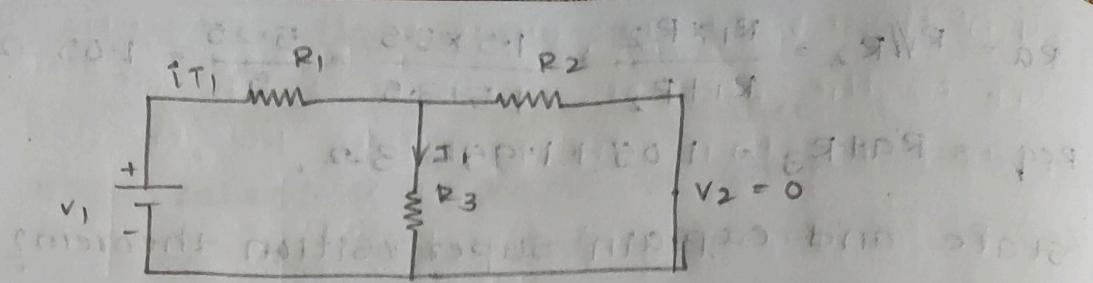
$$\frac{V_1 R_2 + V_2 R_1}{R_1 R_2 + R_2 R_1}$$



$$i_T = \frac{V}{R_T}$$

$$R_T = \frac{V_1}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$$


$$\Rightarrow \frac{V_1 (R_2 + R_3)}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$I' = i_T \times$$

$$i' = \frac{V_1 (R_2 + R_3)}{R_1 R_2 + R_2 R_3 + R_3 R_1} \times \frac{R_2}{R_2 + R_3}$$

$$i' = i_T \times \frac{R_2}{R_2 + R_3}$$
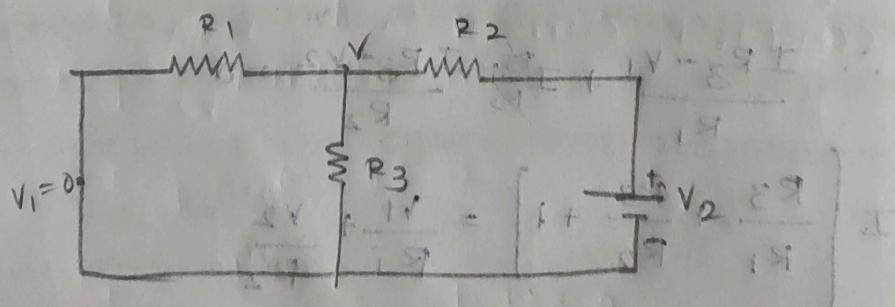
$$i' = \frac{V_1 R_2}{R_1 R_2 + R_2 R_3 + R_3 R_1} + \frac{V - V_1}{R_2 + R_3}$$



$$i_{T2} = \frac{V_2}{R_T}$$

$$i_{T2} = \left( \frac{V_2}{R_2 + \frac{R_1 R_3}{R_1 + R_3}} \right)$$

$$i_{T2} = \frac{V_2}{R_2 + \frac{R_1 R_3}{R_1 + R_3}}$$

$$i_{T_2} = \frac{V_2(R_1 + R_3)}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$i'' = \frac{V_2(R_1 + R_3)}{R_1 R_2 + R_2 R_3 + R_3 R_1} \times \frac{R_1}{(R_1 + R_3)}$$


$$i' = \frac{V_2 R_1}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$I = i' + i''$$


$$I = \frac{V_1 R_2}{R_1 R_2 + R_2 R_3 + R_3 R_1} + \frac{V_2 R_1}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$I = \frac{V_1 R_2 + V_2 R_1}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

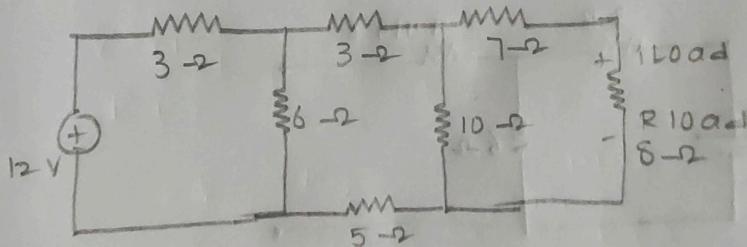(b) find load current through load resistor  
using Thevenin's theorem




for S-1 for  $R_{th}$

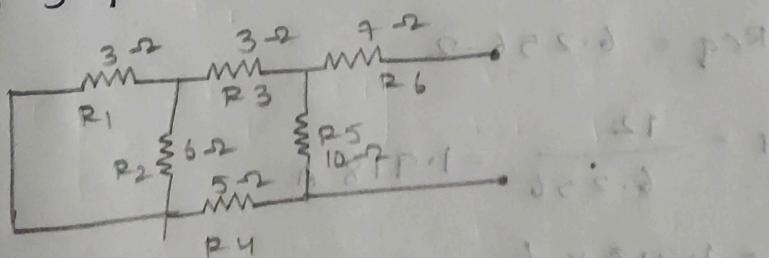

Let


$$R_a = \frac{R_1 * R_2}{R_1 + R_2} = \frac{3 * 6}{3 + 6} = \frac{18}{9} = 2\Omega$$
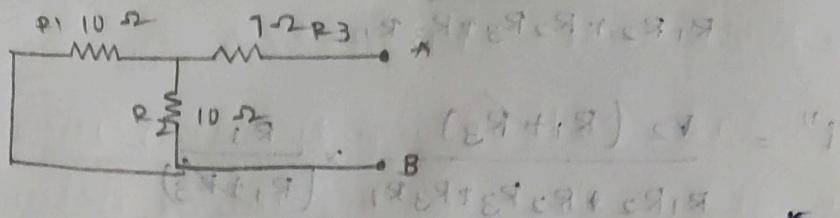
$$R_b = R_a + R_3 + R_4 = 2 + 3 + 5 = 10 \Omega$$



$$R_{th} = \frac{R_1 \times R_2}{R_1 + R_2} + R_3 = \frac{10 \times 10}{10 + 10} + 7 = \frac{100}{20} + 7 = 12 \Omega$$


S-2 for  $V_{th}$

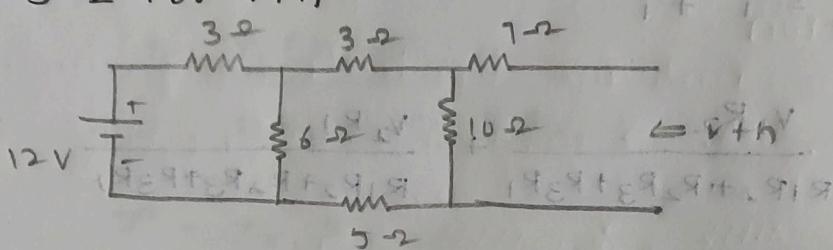

$$I_T = \frac{V}{R}$$

$$R_{eq} = 7//10 + 3 = \frac{7 \times 10}{7+10} + 3$$
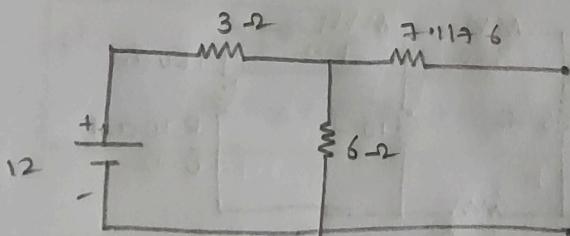
$$= \frac{70}{17} + 3 = \frac{121}{17} = 7.11 \Omega$$



$$R_{eq} = 7.11 // 16 + 3$$

$$R_{eq} = 6.256 \Omega$$


$$I_T = \frac{12}{6.256} = 1.918 \text{ A}$$

$$V_{th} = 1.918 \times \frac{6}{19} = 0.605$$

$$V_{th} = V_{10\Omega} = 0.605 \times 10 = 6.05 \text{ V}$$

7) <sup>15</sup><sub>3</sub> Derive  
function  
excited

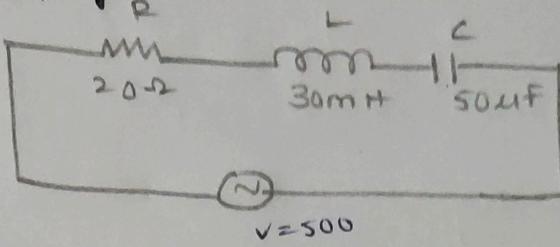Q6) A series connected RLC circuit has  $R=20\Omega$ ,  $L=30mH$ ,  $C=50\mu F$ . calculate the impedance and current when the circuit is excited by 500V 50Hz supply.



Given data

$$R = 20\Omega, L = 30mH, C = 50\mu F, f = 50Hz$$

$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 30 \times 10^{-3} = 9.42\Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 50 \times 10^{-6}} = 63.9\Omega$$

$$Z = R + j(X_C - X_L)$$

$$Z = 20 + j(63.9 - 9.42)$$

$$Z = 20 + j(54.48)$$

$$Z = 58.69.84^\circ$$

$$I = \frac{V}{Z} = \frac{500 \angle 0^\circ}{58.69.84^\circ}$$

$$I = 8.62 \angle 69.84^\circ$$