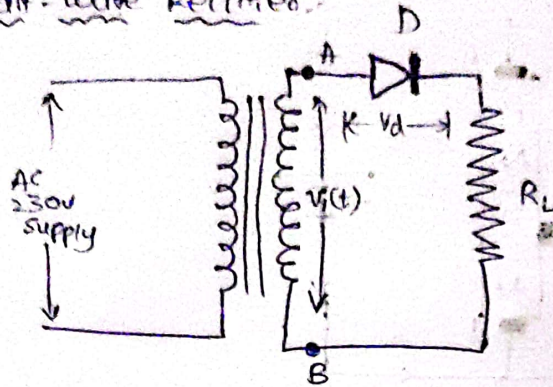


### Unit - 3

(i) Half wave Rectifier.

Ans) Half-wave Rectifier:




- In half wave rectifier, the purpose of the transformer is to step down the input ac supply.
- During the positive half cycle of input voltage, end A becomes positive (+ve) with respect to B. This makes the diode forward biased and hence it conducts current.
- During the negative half cycle of input voltage, end A becomes negative (-ve) with respect to B. This makes the diode reverse biased and it does not conduct current.
- It converts bidirectional to unidirectional.

Disadvantages:

- The output is low.
- Filtering is required to produce steady current.
- $\therefore$  Ripple Frequency =  $1/P$  signal Frequency

Characteristics

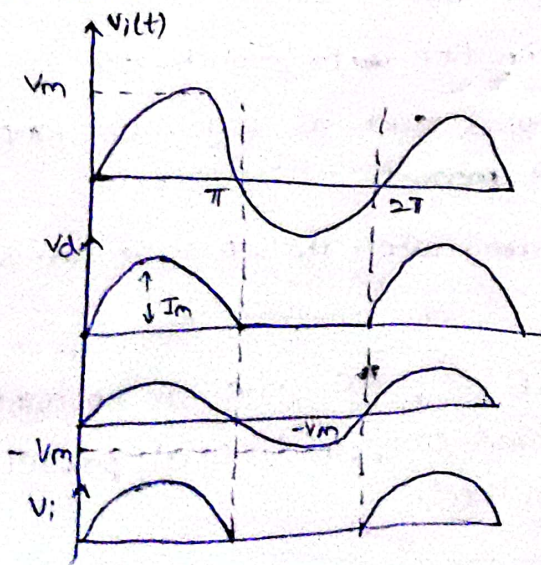



(i)  $0 - \pi$  : Diode - ON

→ Current flows

→ Max. current flows when  $V_i = V_m$

(ii)  $\pi - 2\pi$  : Diode - OFF


→ No current flows

→  $i = 0$ ,  $V_d = -V_m$

$$\therefore I_m = \frac{V_m}{R_f + R_L}$$

2) Full wave Rectifier.

Full-wave Rectifier

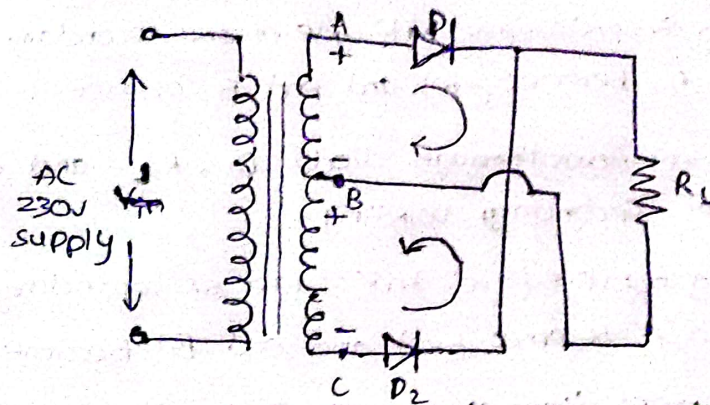

→ In Full wave Rectifier (FWR), current flows through load in the same direction for both half cycles of  $V_p$  ac voltage. This can utilise both half cycles of  $V_p$  ~~ac~~ ac voltage to produce DC output.

→ For positive half-cycle of input voltage, one diode supplies current to load and for the 've' half cycle, of input other diode supplies current to the load in the same direction.


→ There are two types of full wave Rectifier.

(i) Centre-Tapped (FWR)

(ii) Full-wave Bridge Rectifier.




## i) Centre-Tapped FWR:

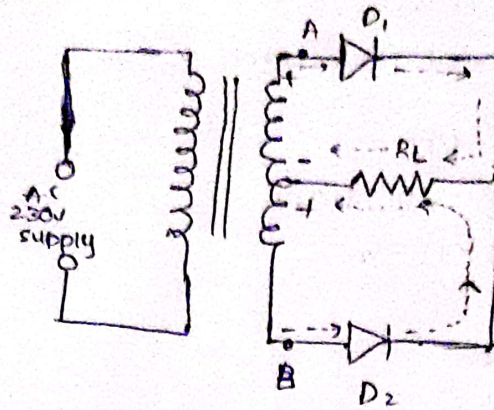

- A centre tapped transformer is used to establish the input signal across each section of the secondary transformer.
- During the positive (+ve) half cycle of the secondary voltage, the end 'A' becomes (+ve) and end B becomes (-ve).
- The current flows through diode  $D_1$ ,  $R_L$ , and upper half of secondary winding.
- During negative (-ve) half cycle of secondary voltage, the end 'A' becomes (-ve) and end B becomes (+ve).
- The current flows through the diode  $D_2$ ,  $R_L$  and lower half of secondary winding.

## ii) Full-Wave Bridge Rectifier:

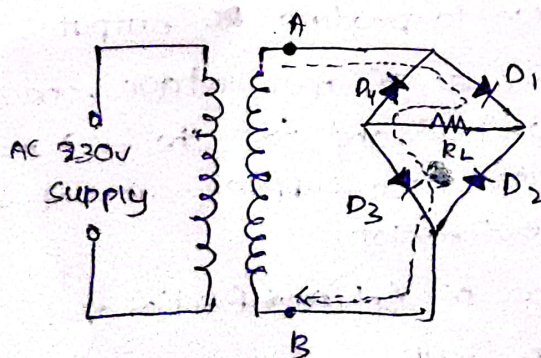

- The need of centre tapped transformer is eliminated in bridge rectifier.
- During positive (+ve) half cycle of secondary voltage,



- the end 'a' becomes (+ve) and end 'b' becomes (-ve).
- Therefore, the diodes  $D_1$  and  $D_3$  conduct so that current flows from 'A' to 'B' through  $R_L$ .
  - During negative half cycle of secondary voltage, the end 'A' is (-ve) and end 'B' is positive (+ve).
  - Therefore, the diode  $D_2$  and  $D_4$  conduct, so that current flows from 'B' to 'A' through  $R_L$ .